

By the end of 1974, we had the "Bean" RMS gain Control, and not much else

"The Race was on"

Jack committed the funds, and I committed the time to show a new Product at the April, 3 1975 National Association of Broadcasters Convention in Las Vegas!!!

We needed to design and build a "complete" limiter less than 3 months!
Not possible,

So, we came up with a scheme the could produce a "display "Multi-Limiter that would function

The Circuitry would be on Wire-wrap cards in a frame mounted in a Display Pedestal
On the top of the Pedestal, would be Dummy Metal, with Meters and fake controls
From the Booth Visitors viewpoint, they would think they saw a completed unit!

As I remember there were two... another with no Guts below, on a second pedestal

This scheme only solved the Visual Problem; something needed to go in the Box; that worked
And could be described in a "One Sheet"... we gave ourselves to the middle of March

The limiter needs many parts, and features to work
And there needed to be two versions, one for AM & one for FM

The sketches show System and Circuit Development




The Puzzle pieces are:

Block Diagram
Input Filtering
Split Frequency Band, RMS Compressor
"Fast Limiter"
AM Signal Processing, Polarity Flipping
FM Signal Processing, Emphasis

The "Blue lines" show what was on the Wire-Wrap Cards in the Pedestal

MultiLimiter, very early Concept Drawing
From DEC1974 or JAN1975

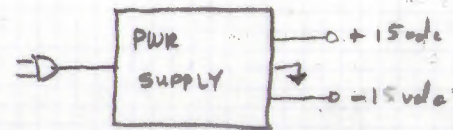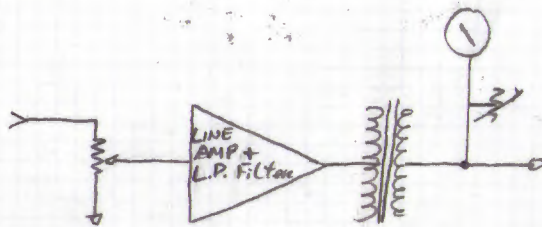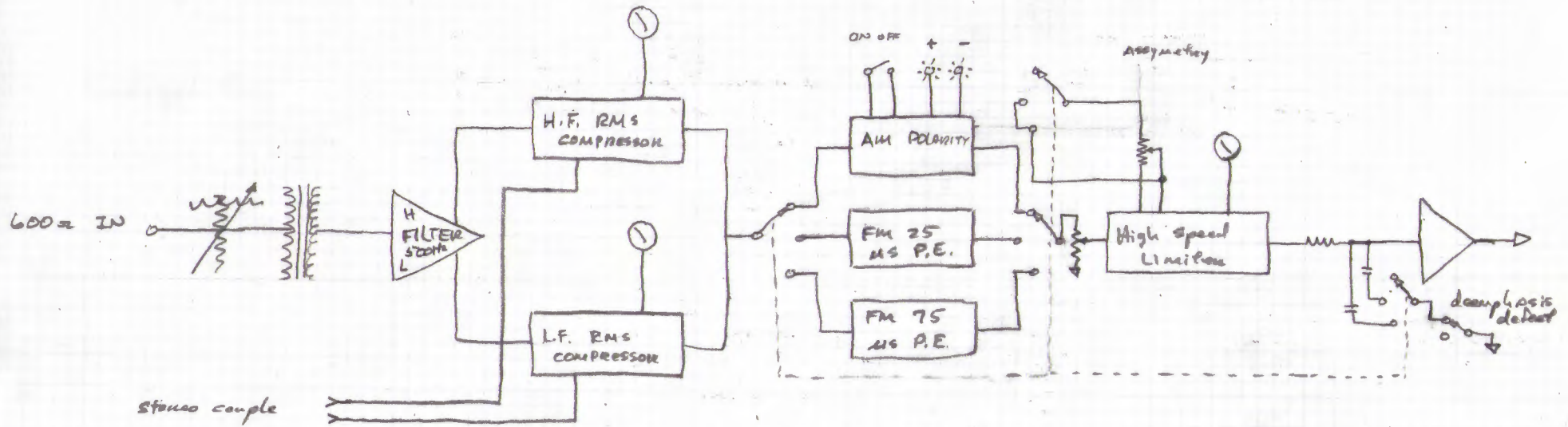Notice, one box does it all, AM & FM
Also "Split Band", frequency domain RMS processing



For proper operation, extraneous audio must be filtered out

Components such as Low Frequency A/C sounds, Needle Drops (Remember phonograph Records?)
Also some Stations/Networks used low frequency Keying 20 to 40Hz...

The High Pass Filter is of a Standard Design

The only difference being the inductors are replaced with simulated inductors (Gyrators)


The initial Design was for a cutoff of 50Hz

Later reduced to 40 Hz


And later increased to 90Hz for better RMS performance, and better transmitter efficiency

Low pass filter. Sharp cutoff.

19 KHz --- notch.

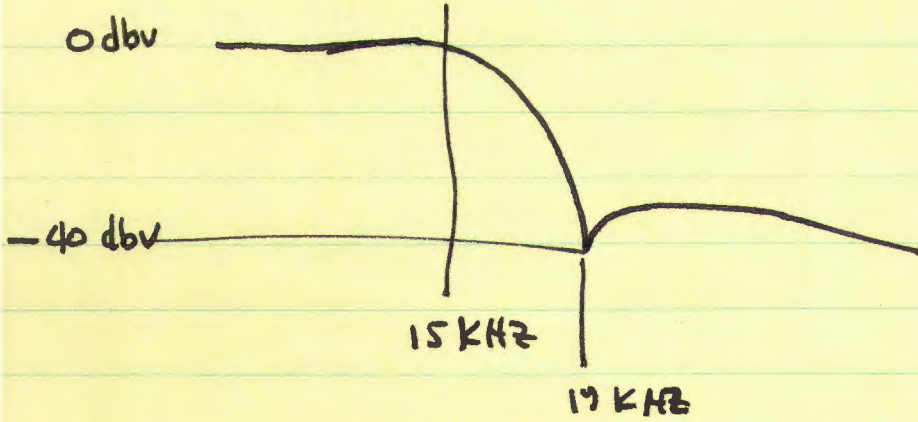

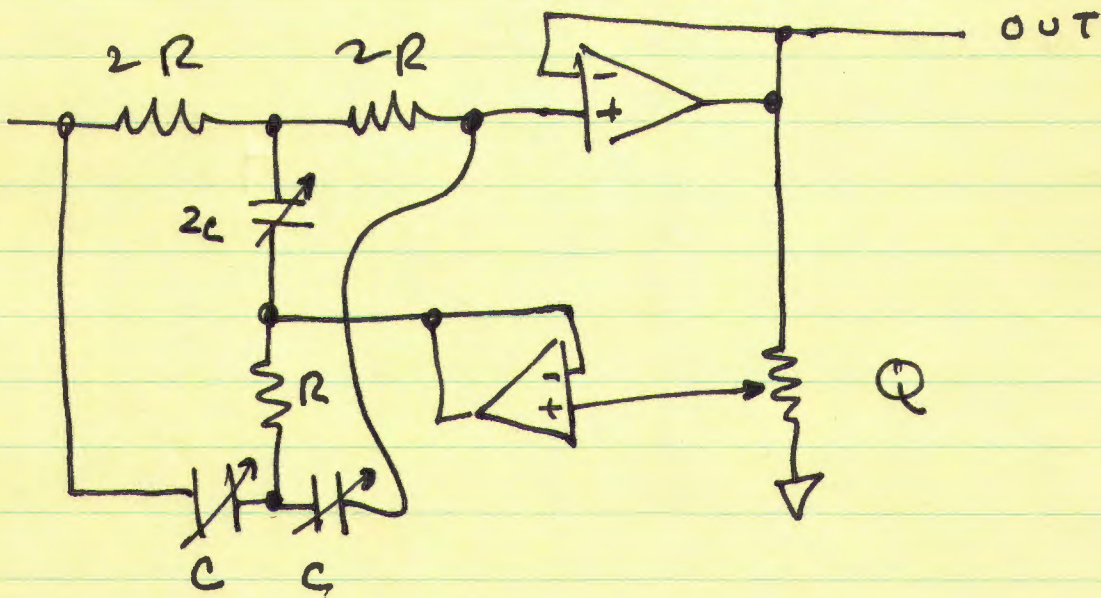
for Consider - first a notch filter
15 KHz 19 KHz




where $f = \frac{1}{2\pi RC}$ let $C = .001$?

$R = \frac{1}{2\pi f C} = 8376.58 \Omega$ ok ...

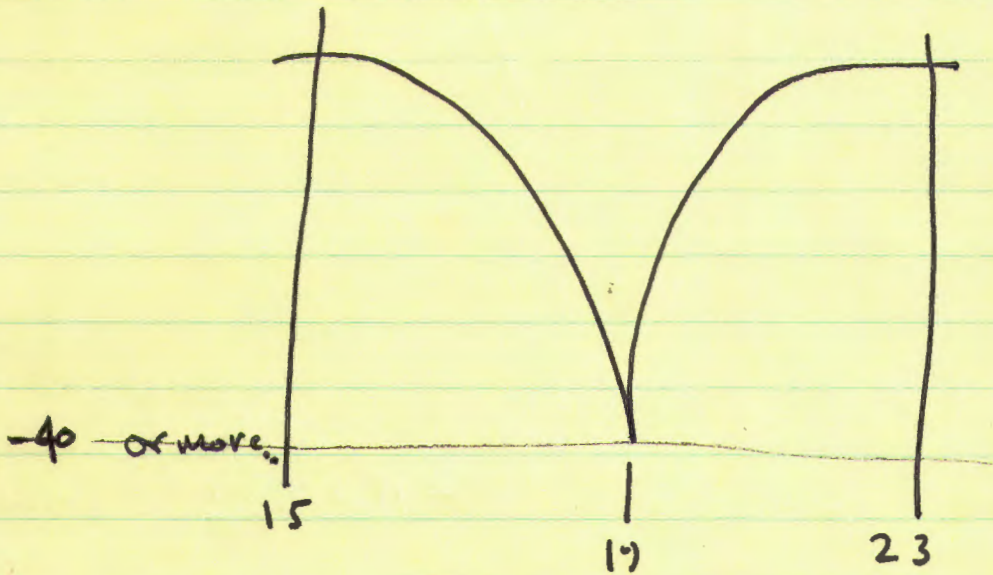Try Notice this could give
us a notch... with symmetrical
sides... - say a depth of 40 db.




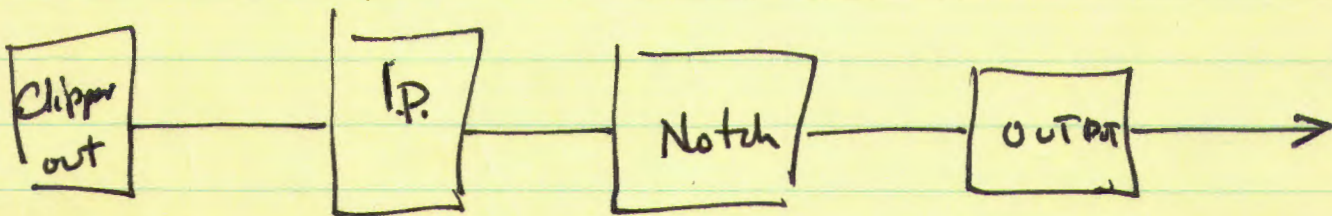to help... other low pass.. filter
Suggest ..




High Low pass at least 40 db/octave..

filter section

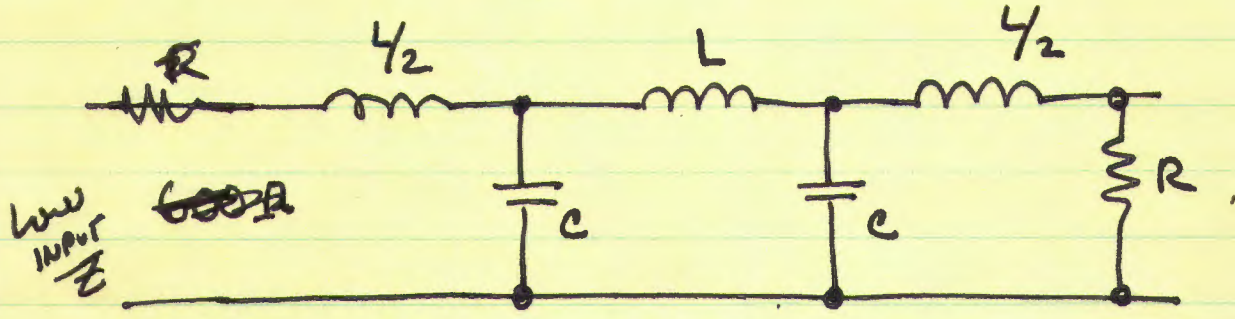

$$L = \frac{R_0}{\pi f_c}$$

$$C = \frac{1}{\pi f_c R_0}$$

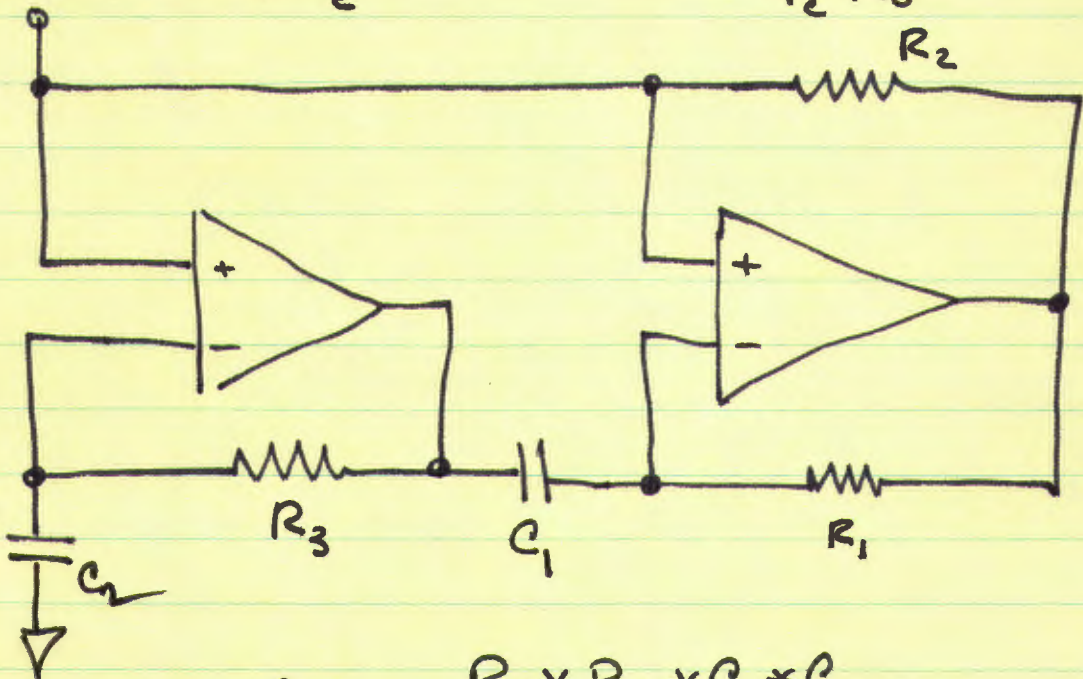

$$C_R = \frac{R_1 * R_3 * C_1 * C_2}{R_2}$$

let $R_1 = R_2 = R_3$ and $C_1 = C_2$
then

$$C_R = \boxed{RC^2}$$


④

let $L = 2000$ henrys.

then $R_0 = L\pi f_c = 2000\pi 15000 = 9.42 \times 10^7$

$$C = \frac{1}{\pi f_c R_0} = \frac{1}{\pi \times 15000 \times 9.42 \times 10^7} = 2.25 \times 10^{-13}$$

Eq. circuit

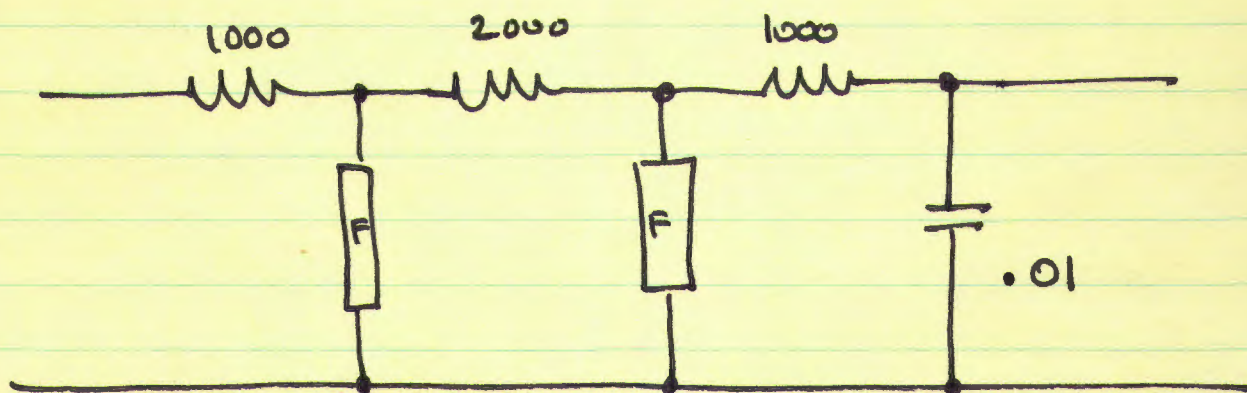

for (F)

let $C = .1$ or 10^{-7}

$$R = \frac{C_R}{C^2} = \frac{2.25 \times 10^{-13}}{10^{-14}} = 22.5 \Omega$$

let $C = .01$

$$R = \frac{C_R}{C^2} = \frac{2.25 \times 10^{-13}}{10^{-6}} = 2250 \Omega$$

Try


50 cps

~~low~~

High Pass

(1)

JAN 1975?

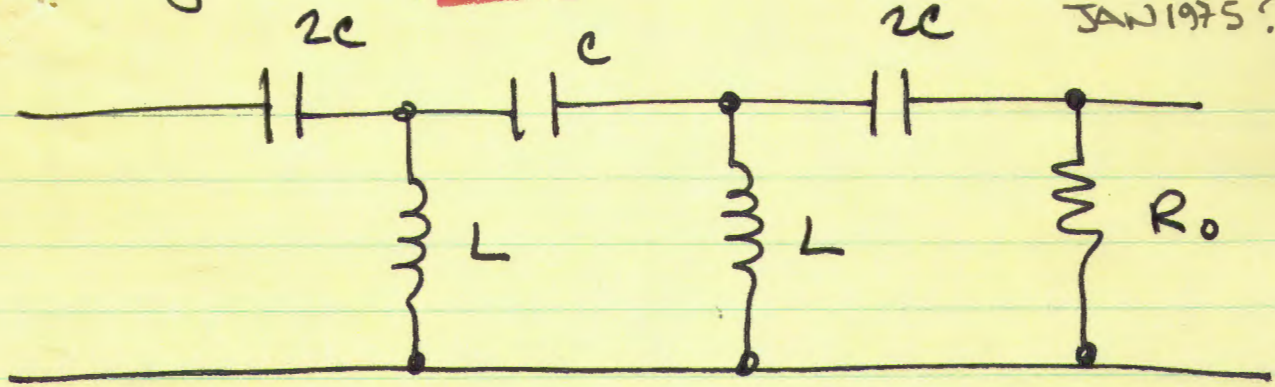

where $C = \frac{1}{4\pi f_c R_0}$

and

$$L = \frac{R_0}{4\pi f_c}$$


let $C = .1 \text{ mfd}$ $2C = .2 \text{ mfd}$

$$R_0 = \frac{1}{4\pi f_c C} = \frac{1}{4\pi * 50 * (10^{-7})} = \underline{15.9 \text{ K}}$$

$$L = \frac{15.9 \text{ K}}{4\pi * 50} = 25.3 \text{ henrys.}$$

(2)

for L use a gyrator circuit.

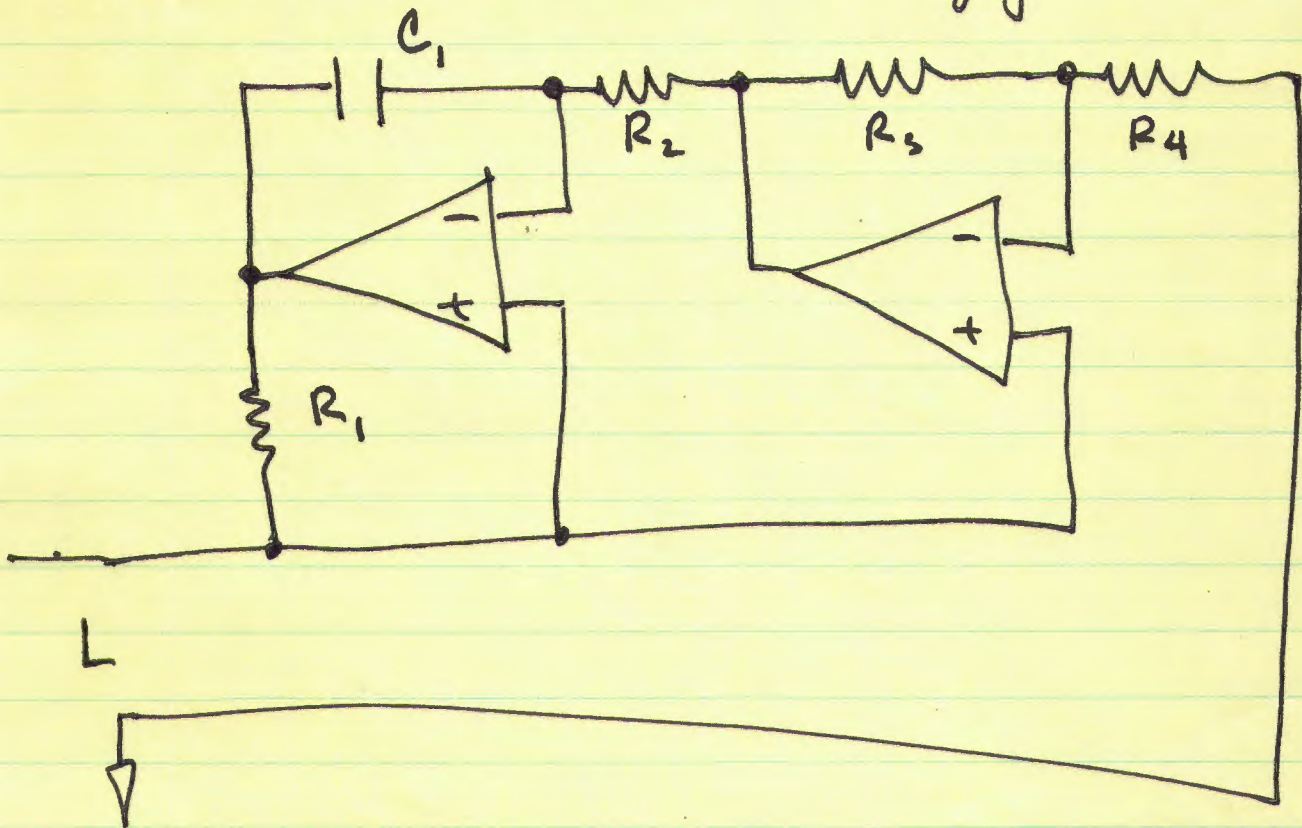

$$\text{where } L = \frac{R_1 * R_2 * R_4 * C_1}{R_3}$$


~~where~~ let $R_1 = R_2 = R_3 = R_4$

then $L = R^2 C$

Let $C = .1 \text{ mfd.}$

then $R = \sqrt{\frac{L}{C}} = \sqrt{\frac{25.3}{10^{-7}}} = \underline{15.9 \text{ K}}$

Try this circuit...

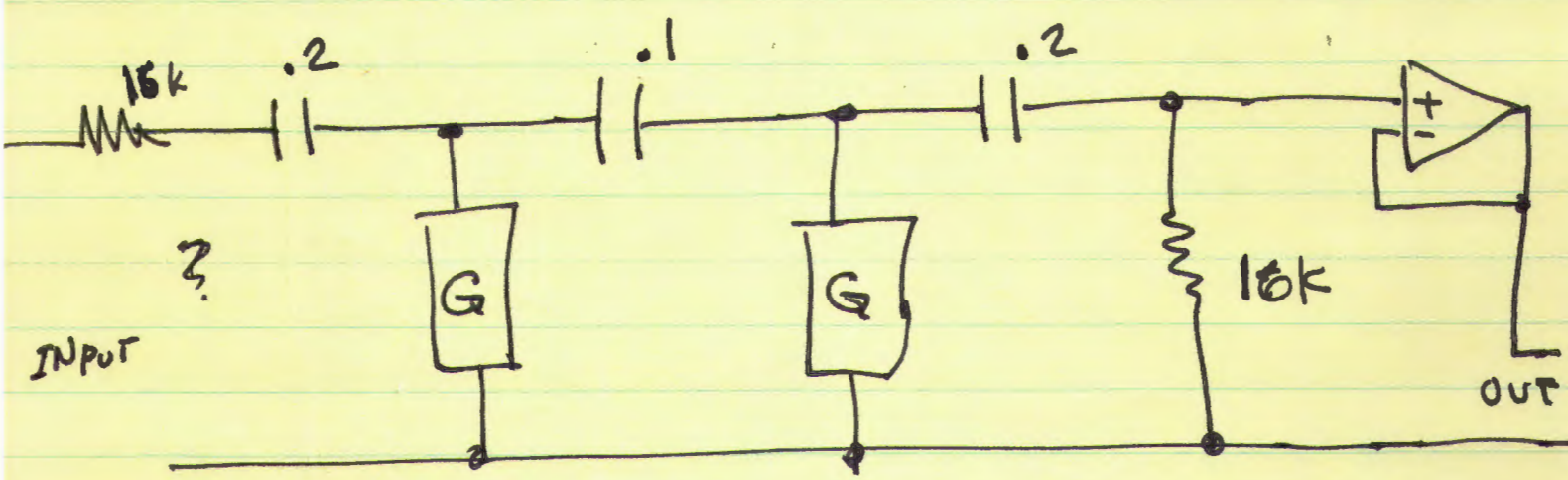

Works extremely well...!!!


however - cutoff freq. is too high.
to original formulae.

make L larger.. if R_0 larger.
~~C~~ larger. R larger.

choose $R = 10k \Omega$... try

Notice the output high Z .
is $1/2$ the voltage (-6db) of input..
Can be made up in follower.

Gyrator High pass filter

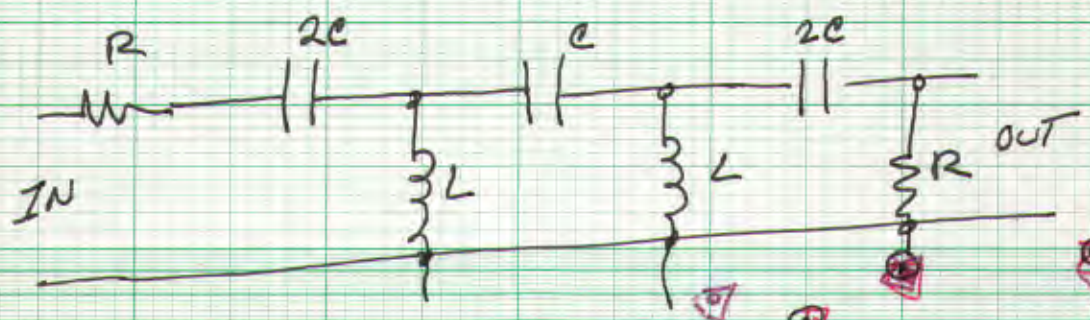


EMF 1
VOLTS

Semi-Logarithmic
4 Cycles x 10 to the inch


R 2470-SL-4
MADE IN U.S.A.
VERNON
FIX LINE

.01


.001

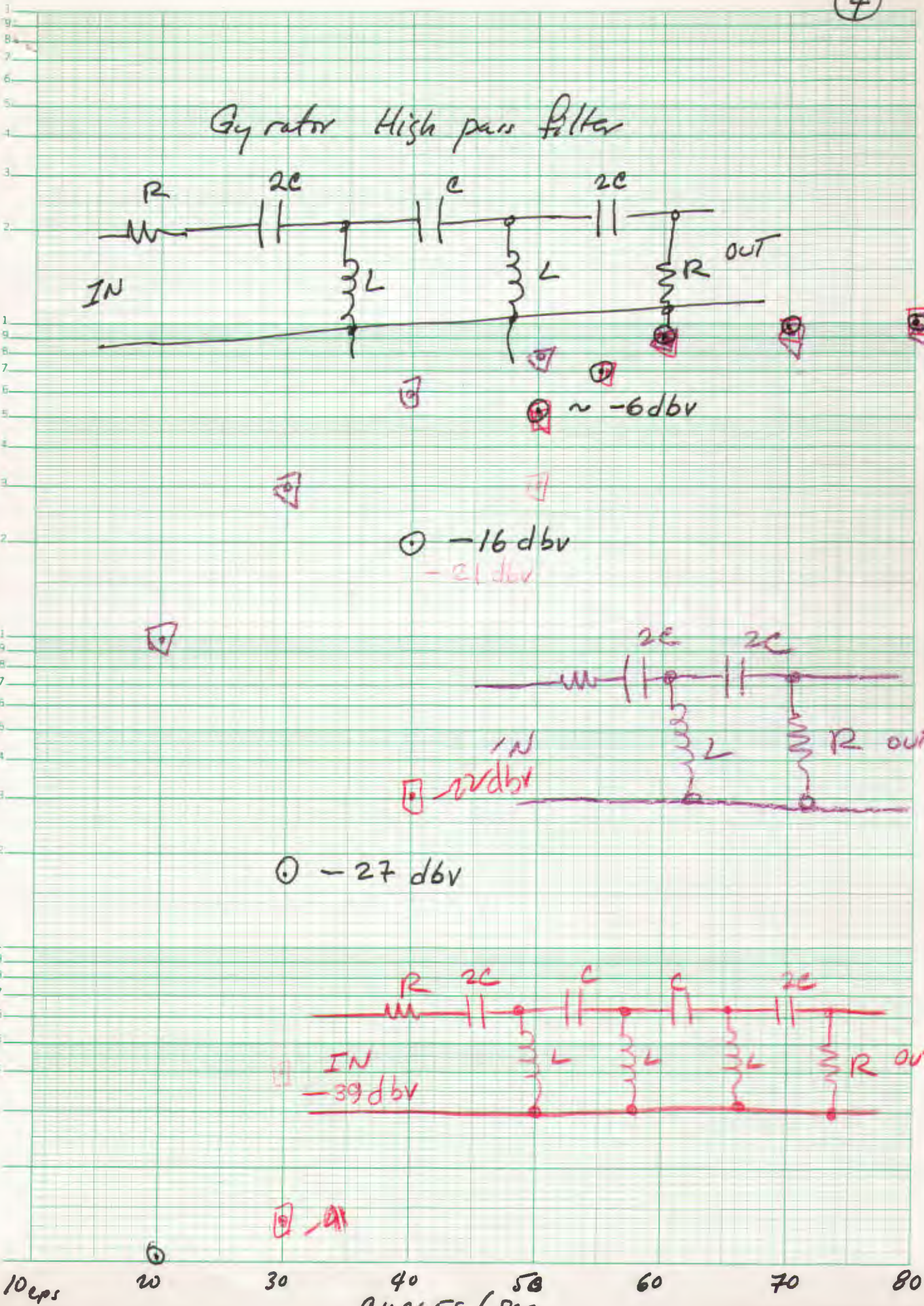

~ -6 dbv
 -16 dbv
 -21 dbv

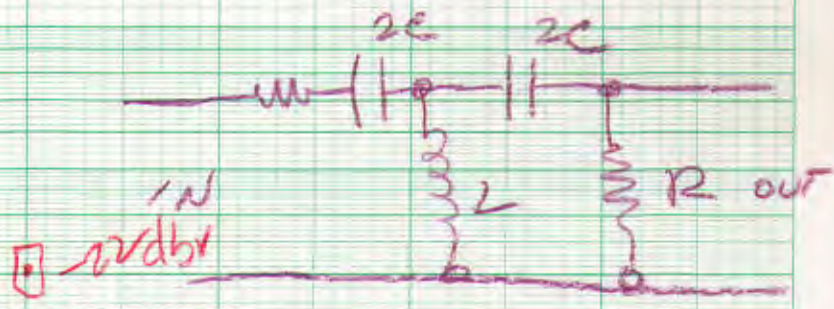

-27 dbv

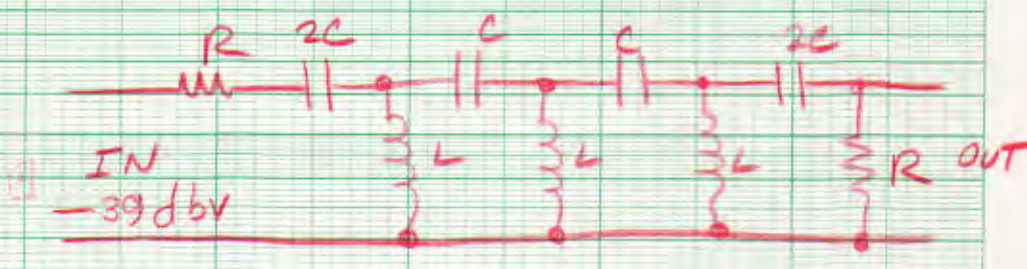


-39 dbv

-41


10 cps 20 30 40 50 60 70 80
CYCLES / SEC

Suggest Circuit

Good to $\sim 30\text{KHz}$,

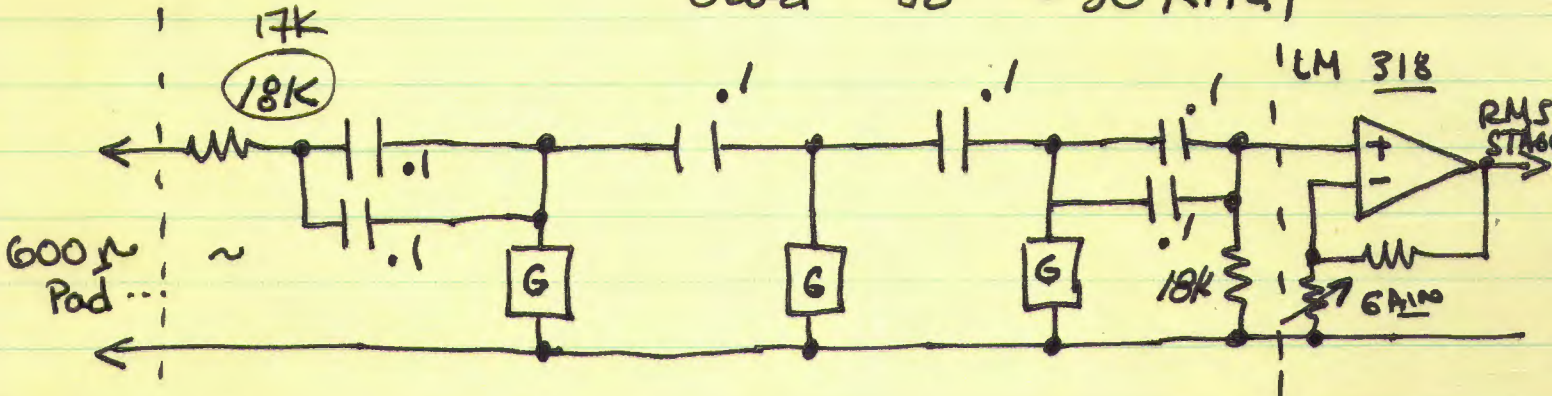

Byrator Sections...

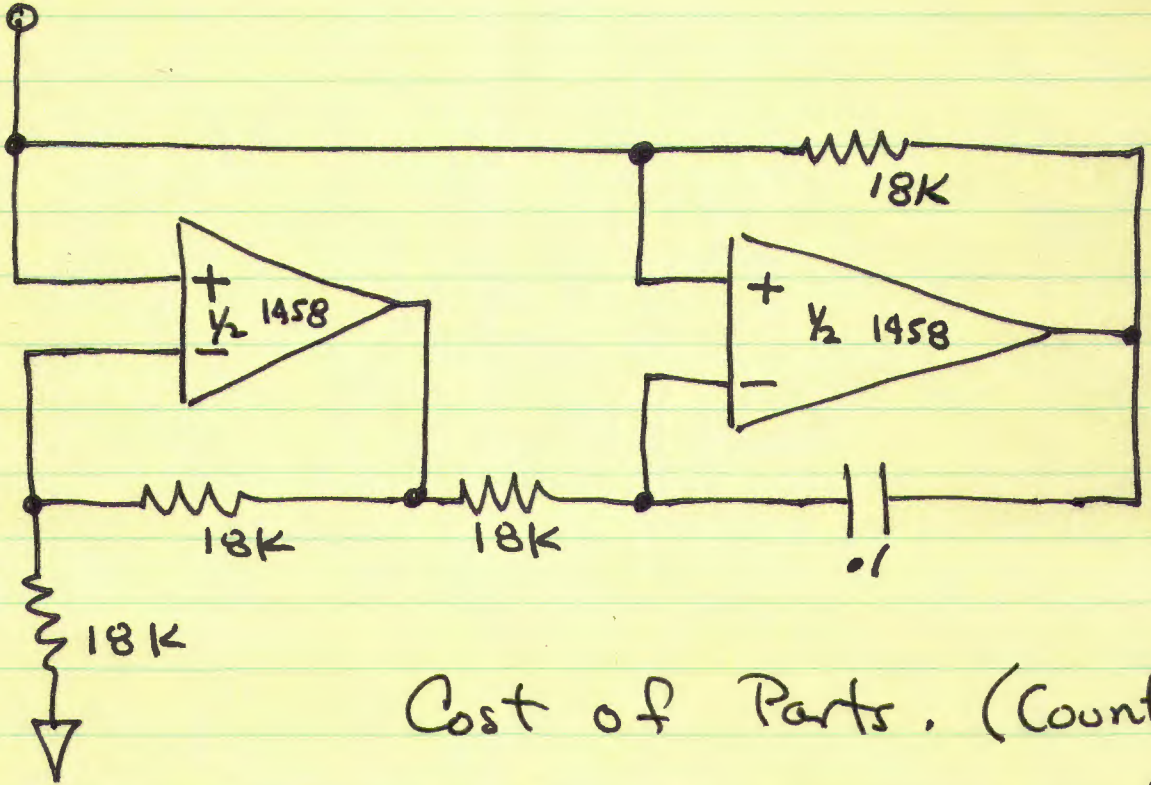


Cost of Parts. (Count)

14	-	18K Ω	\sim	56
9	-	.1 mfd	\sim	1.80
3	-	1458	\sim	2.25
				4.61


under \approx \$5.00 \approx

6

High Pass filter.

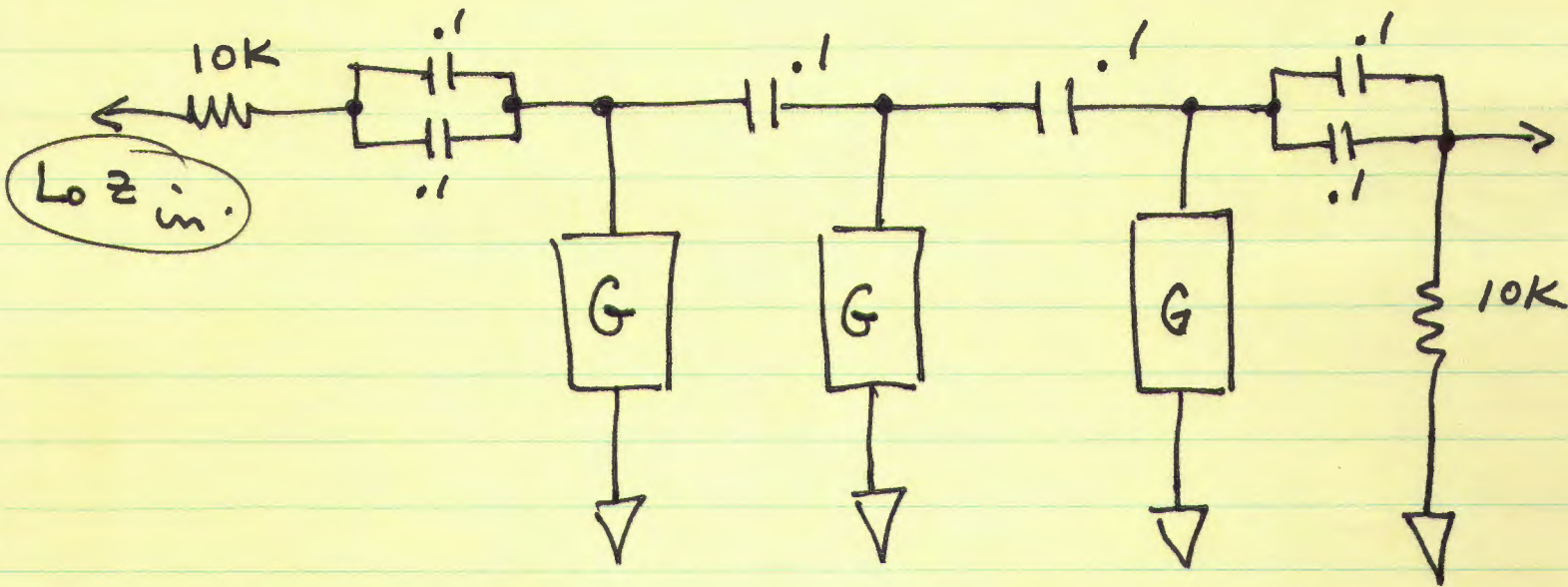

Gyrator... Aprox. -7 db.. in passband.

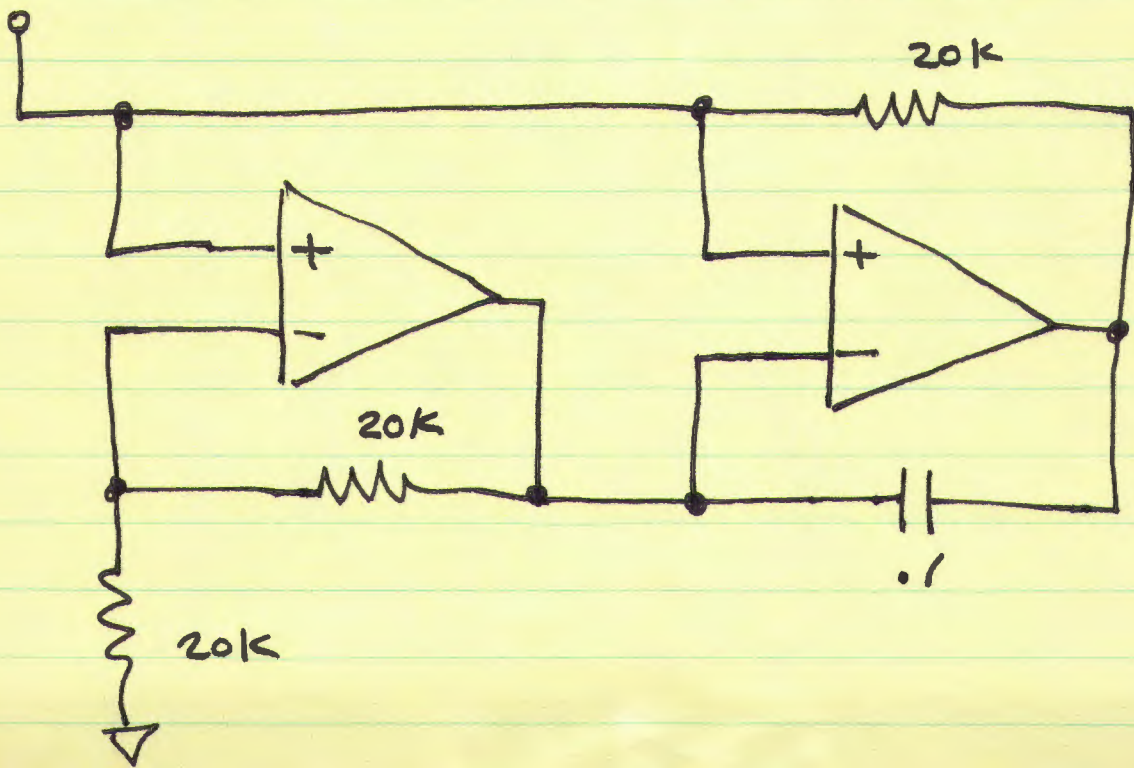

Split frequency Band RMS compression was the norm in 1975
The initial design used this technique

Separating the 'Low' and 'High' frequencies in the processing chain, and combining later has several advantages (and disadvantages)


Consider two audio tones of similar amplitude, one at 100Hz the other at 1000Hz
The two tones sum, the 1000Hz tone appears to 'ride' on the 100Hz tone

The Level Detection would see the envelope, of the composite signal and compress more than desired... that is the amount of compression would depend on the frequency content... not desirable here...
Only necessary in the Limiter stages...

By splitting the Frequency Bands this characteristic can be somewhat improved
At the expense of adding coloring the summed audio

Band split for R.M.S. limiter
 will ~~use~~ state variable filter at
 center freq. of 600 cps. ①

where circuit \rightarrow is

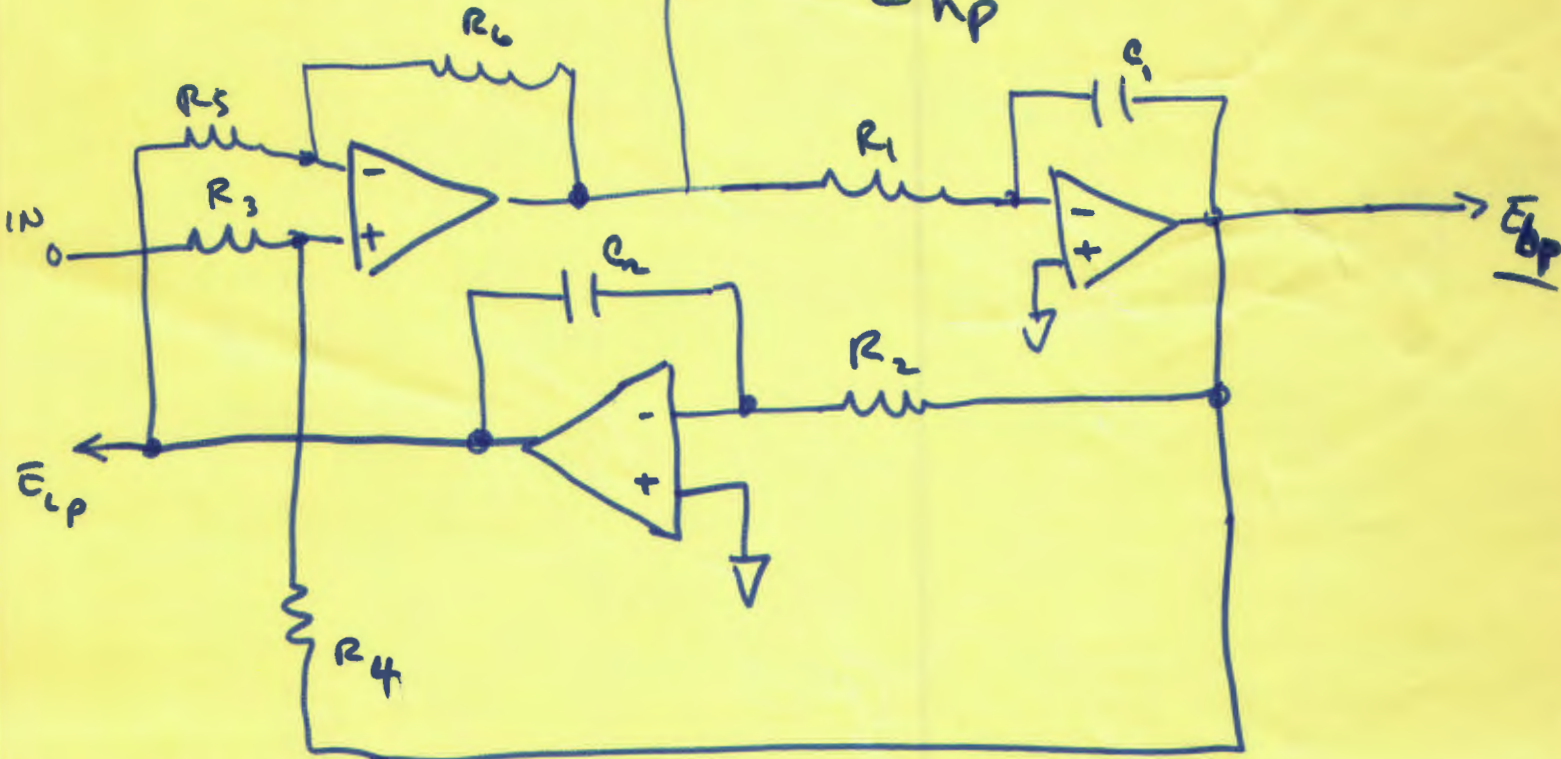

with formulae:

$$H_0 = \frac{R_4}{R_3}$$

$$\omega_0 = \left(\frac{R_6}{R_5 R_1 C_1 R_2 C_2} \right)^{1/2}$$

$$Q = \frac{1}{2} \left(\frac{1 + R_4/R_3}{1 + R_6/R_5} \right) \left(\frac{R_6 R_1 C_1}{R_5 R_2 C_2} \right)^{1/2}$$

if we choose $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R$
 and $C_1 = C_2 = C$

We have:

$H = 1$ - Gain of 1 ok

$\omega_0 = \left(\frac{1}{R^2 C^2}\right)^{1/2} = \frac{1}{RC}$

$Q = 1$ ok

we would like a freq. of 600 cps

or $\omega_0 = 2\pi f = 3769.91 \text{ rad/sec}$

trial for $R = 10k$

$C = \frac{1}{\omega_0 R} = \frac{1}{3.769 \times 10^3 \times 10^4} = 2.65 \times 10^{-8} = .0265 \mu\text{f}$

ok choose $C = .022 \mu\text{f}$. the R :


$R = \frac{1}{\omega_0 C} \approx 12k \Omega$

Works Good.

must add - h.p. and h.p. function
together. . . .

then when h.p. b.p. and l.p. are
joined there is very little
ripple over entire range.



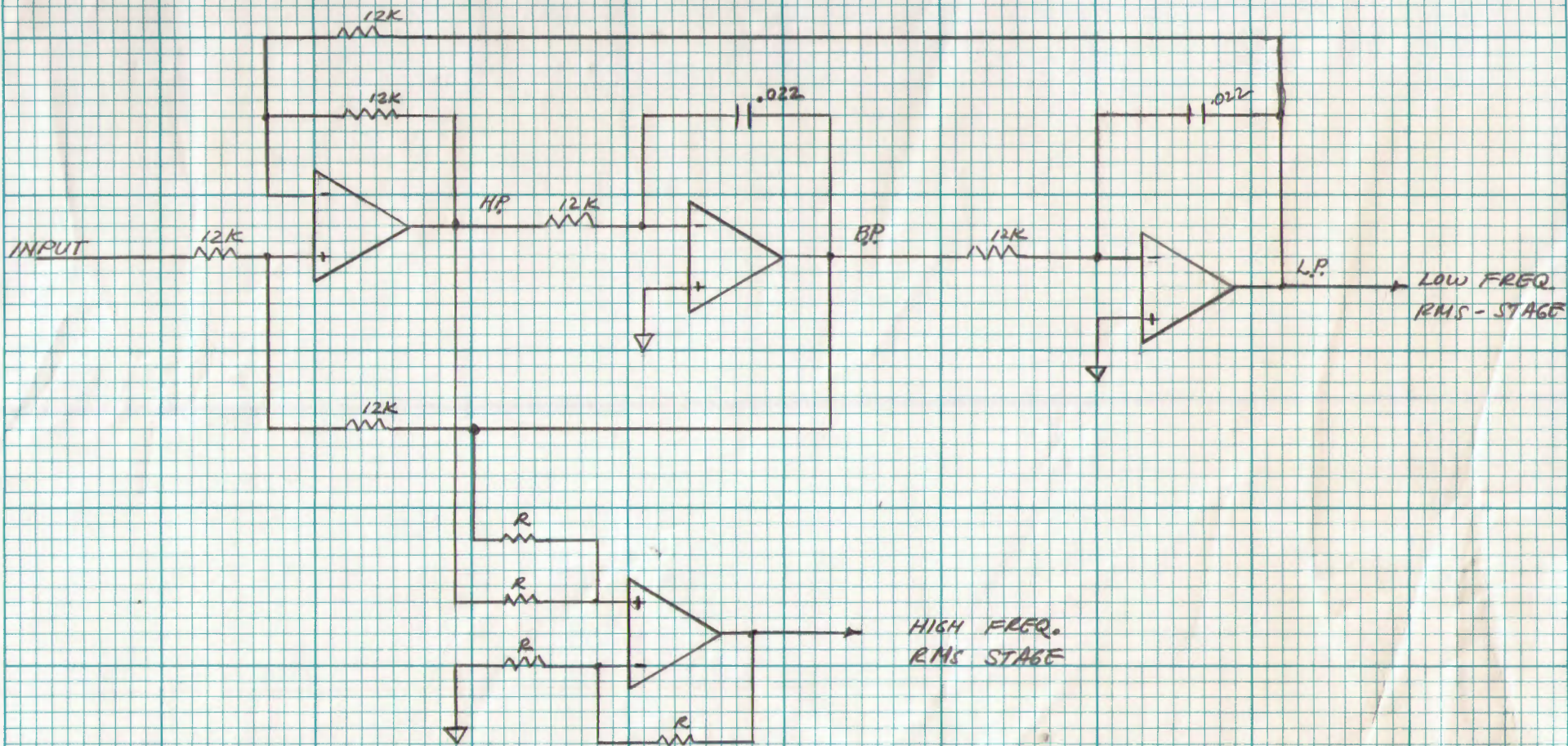
Some drop on high
end probably mismatch
in 10k - resistors.



NOTE - OUTPUTS
MAY BE USED DIRECTLY TO
DRIVE RMS "BEAMS"

FREQ. SPLITTER FOR
SPLIT BAND RMS LIMITER.

PA6 MAY FEB 17, '75

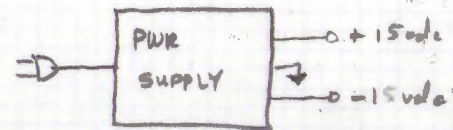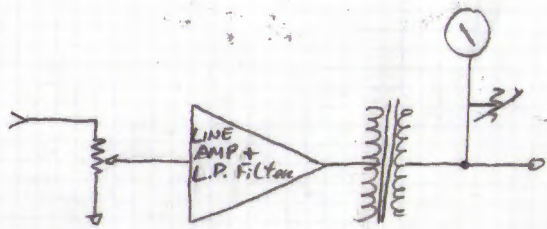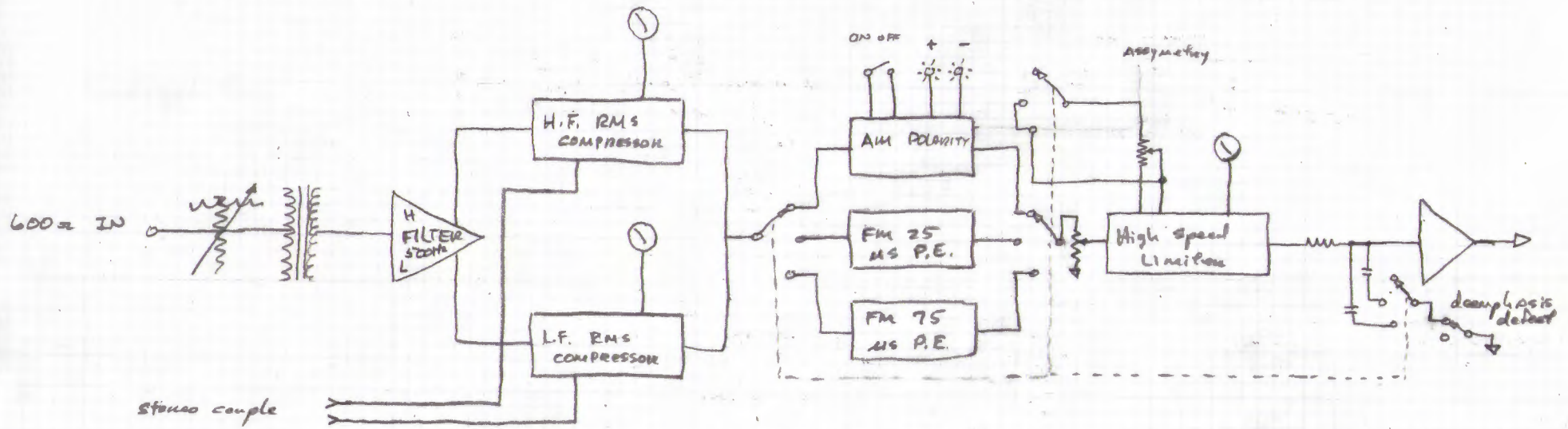

Alignment procedures for Split band -

1. Short input
2. Set both VU meters to zero - or 100%
3. connect sine osc. to input set output to 1 volt P-P
4. Set gain reduction pot to mid range
5. connect oscilloscope (dual trace) L.P. output of filter and and H.P. output of filter -
6. Adjust freq. for equal output of both L.P. and H.P. channels
7. Adjust output of osc. till low freq. VU meter reads ≈ -7 db -
8. Adjust Limit balance till till High freq. VU meter read the same as low freq. VU meter (Balanced - gain reduction)
9. Adjust osc. to 100 cps to read output of -
10. Adjust osc. to 10,000 cps. set freq. balance till for same output as in step 10.
11. adjust output pot to desired level -

The apparent Loudness of the Broadcasted signal is the Peak-to-Average amplitude
The trick is to reduce the amplitude of the peaks, without significantly changing the character
Or adding discernible distortion


The RMS Compressor reduces the Dynamic Range of the inputted signal
So more aggressive techniques may be used to reduce the peak-to-average amplitude

The next step is to take off the peaks... fast by gently ("Contoured Clipping")

I preferred a logarithmic Feed-Forward limiter... easy to implement
Jack preferred the FET Gain Reduction stage, similar to the UREI approach
The latter allow for more control, of attack and release times...

Finding suitable FET's was not easy...
We needed a fairly wide dynamic control range
Without introducing significant distortion, of the overall signal

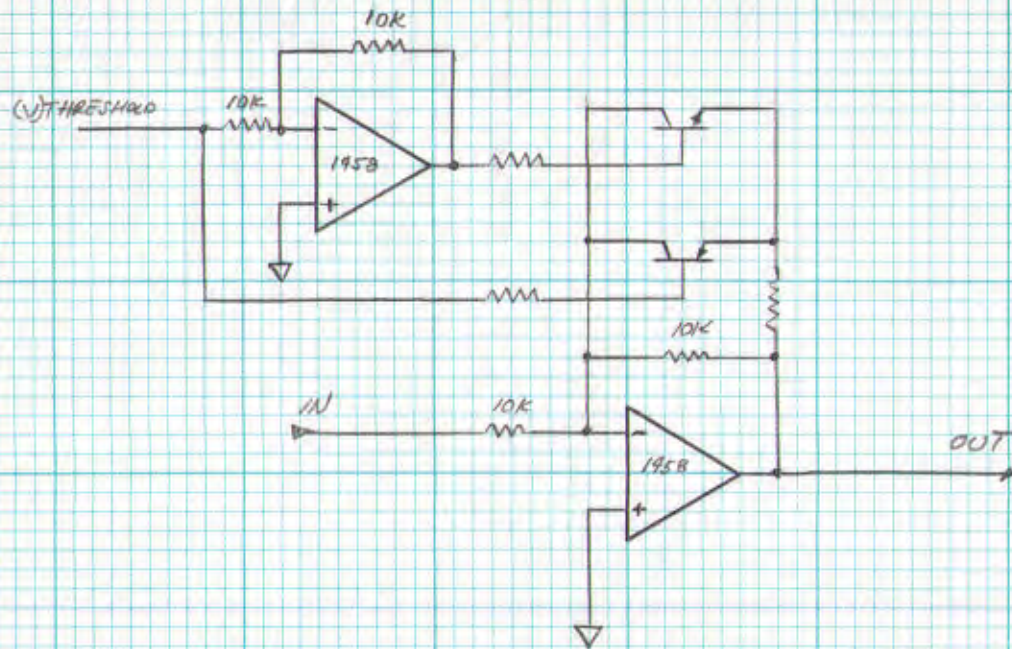The approach I proposed for a 'Fast' control element
Never explored!!!




SYMMETRICAL LOG CLIPPER
PROGRAM FEB 6, 1975


High speed limiter.

Need a limiter - that can "ride the gain" over a small range - and also do peak limiting.

Suggest

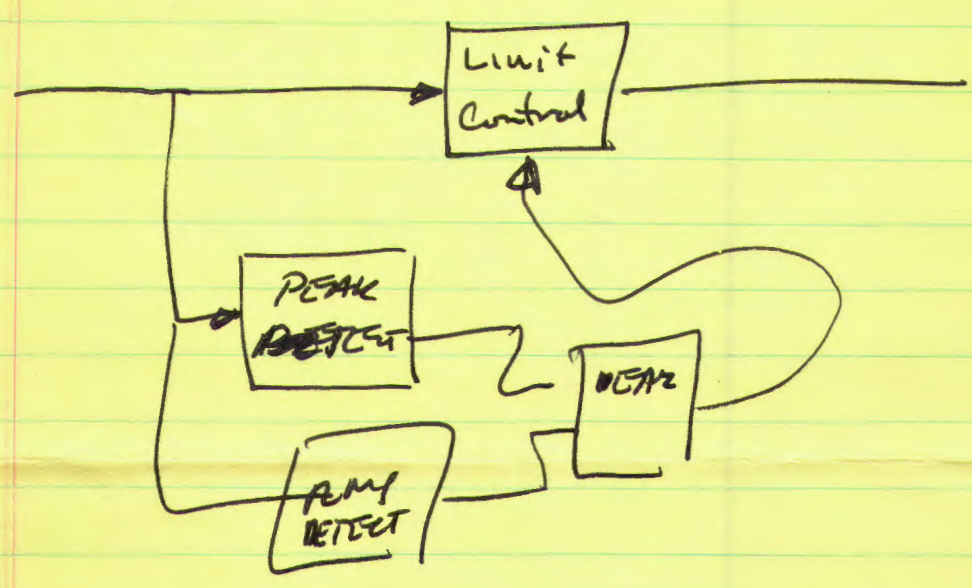


Schematic - limit control

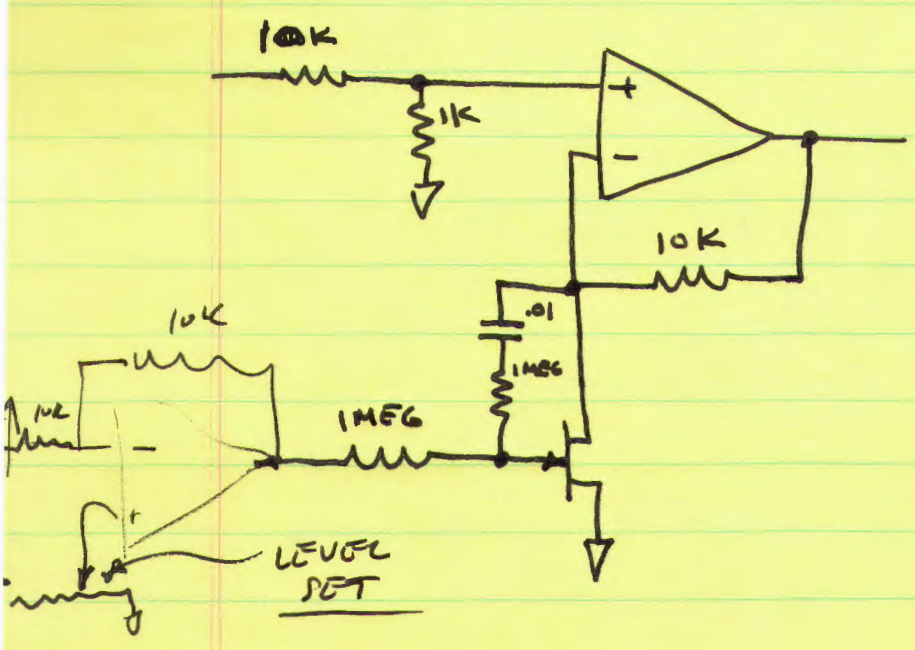



Using a simple average controller - i.e. full wave rect. and filtering - tracking is hard to achieve... however level set does work satisfactorily

try - peak detector. and average detector such that input looks like -

1

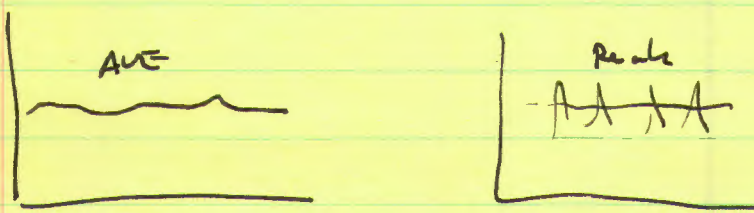

thus feed to control.

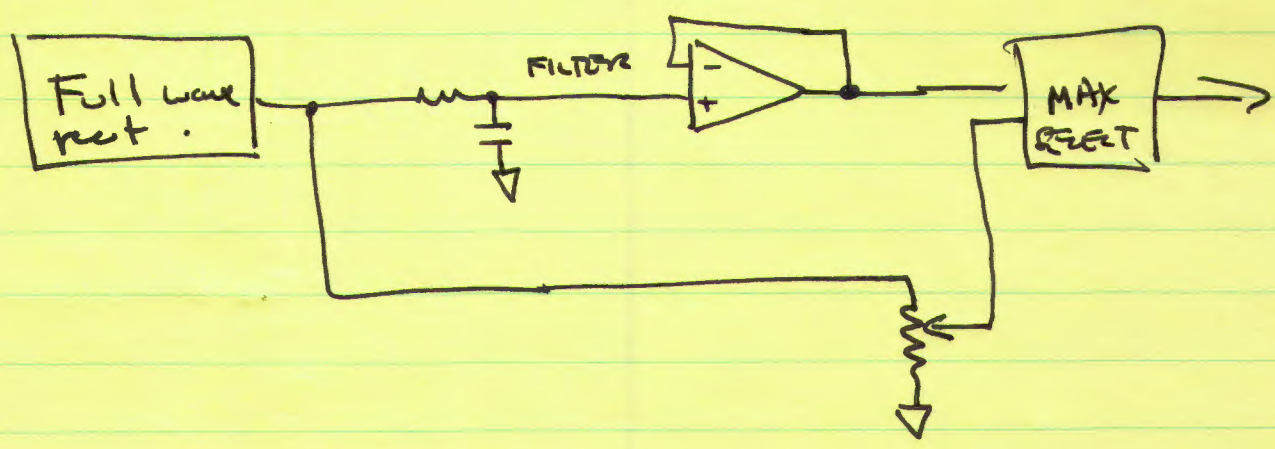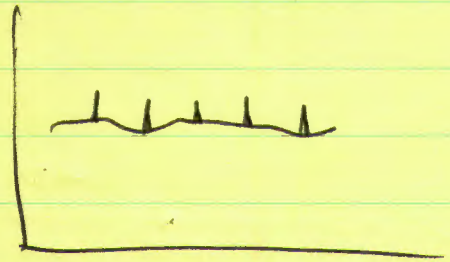

Circuit seems to work ok -

Problem seems to be
non-linear ~~FET~~ age.

- also need to work on

ave. attack timing. -


and peak threshold and
loop gain -

As the feedback resistor
increases

Several circuit were tried
 - one using feed back
 proved to be most interesting
 gain - exp. and comp. were
 excellent. however peak
 limiting was very hard to
 achieve ..

Tash to. came up with
 a new circuit which may
 require further development.

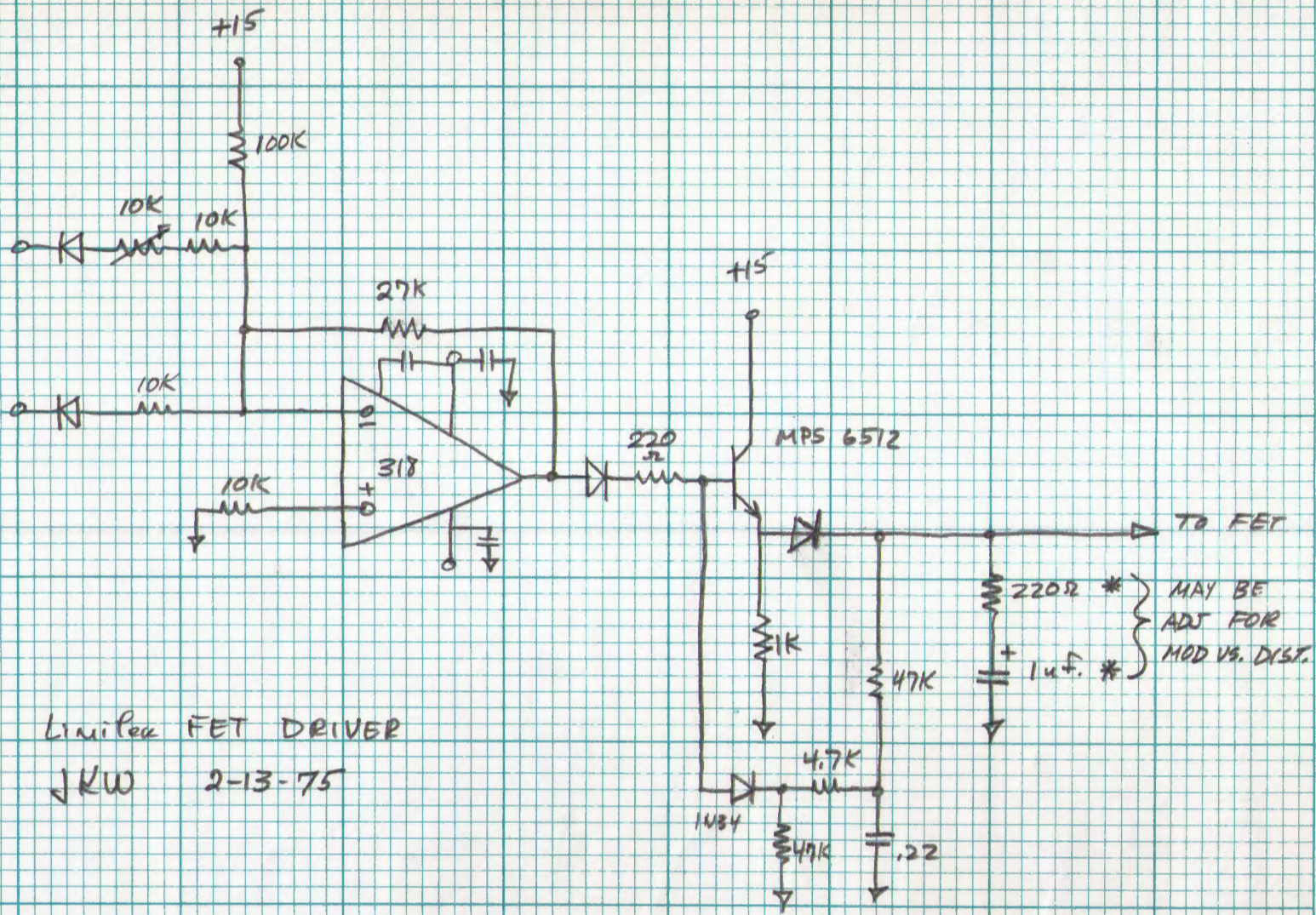
Will go with Tash's
 circuit
 only ~~resistor~~ in
 network changed to ~~base~~
 3 diode (1N919 drops)




Limited FET DRIVER


JKW 2-13-75

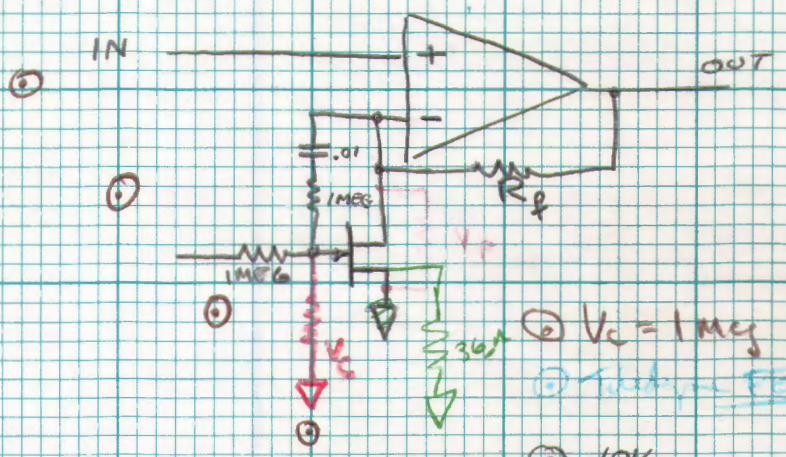VOLTAGE CONTROL VERSUS
 OUTPUT (GAIN) FET CONTROLLED
 AMP



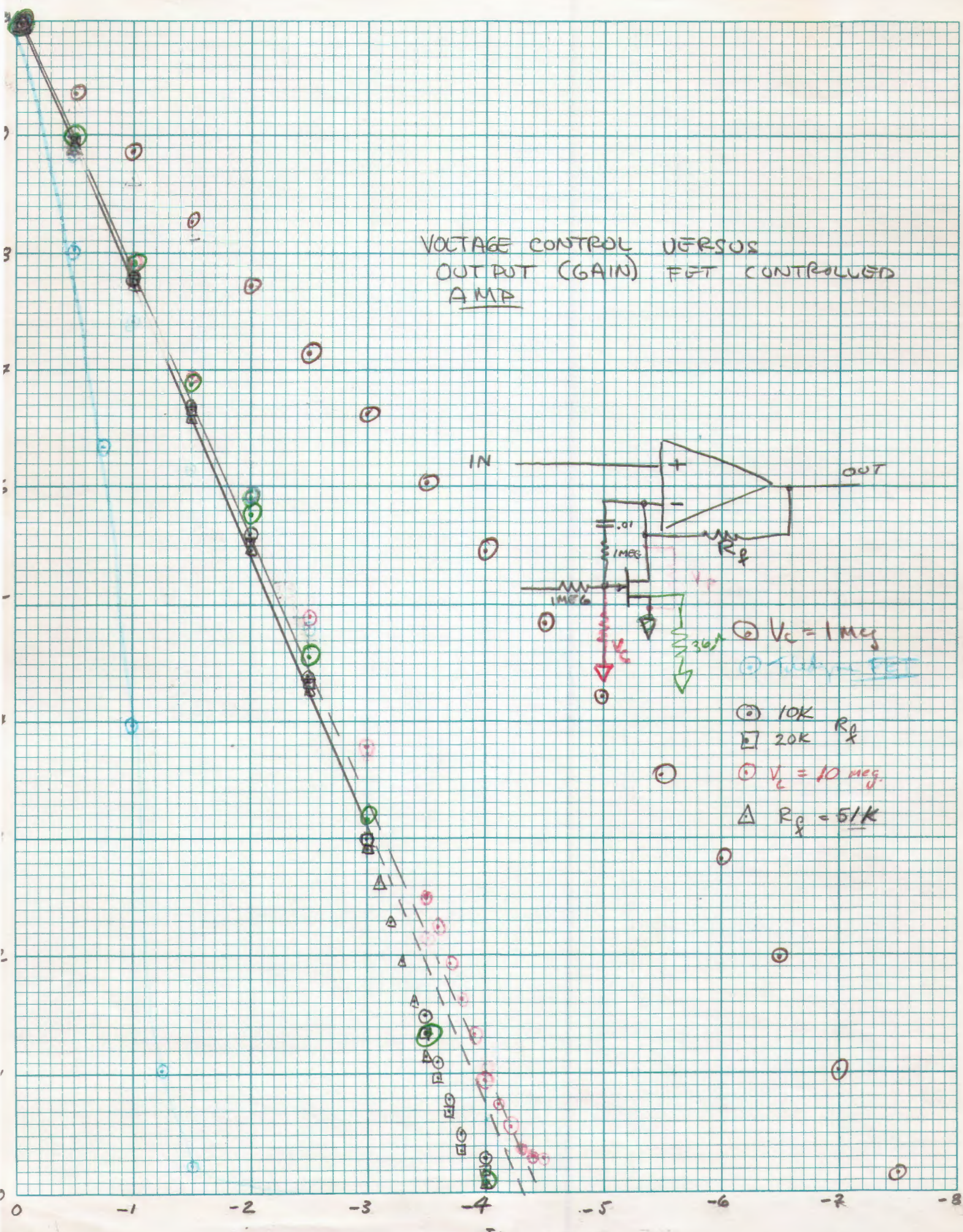
- $V_c = 1 \text{ meg}$
- $V_c = 10 \text{ meg}$
- $R_f = 10 \text{K}$
- $R_f = 20 \text{K}$
- $V_L = 10 \text{ meg}$
- △ $R_f = 5 \text{K}$



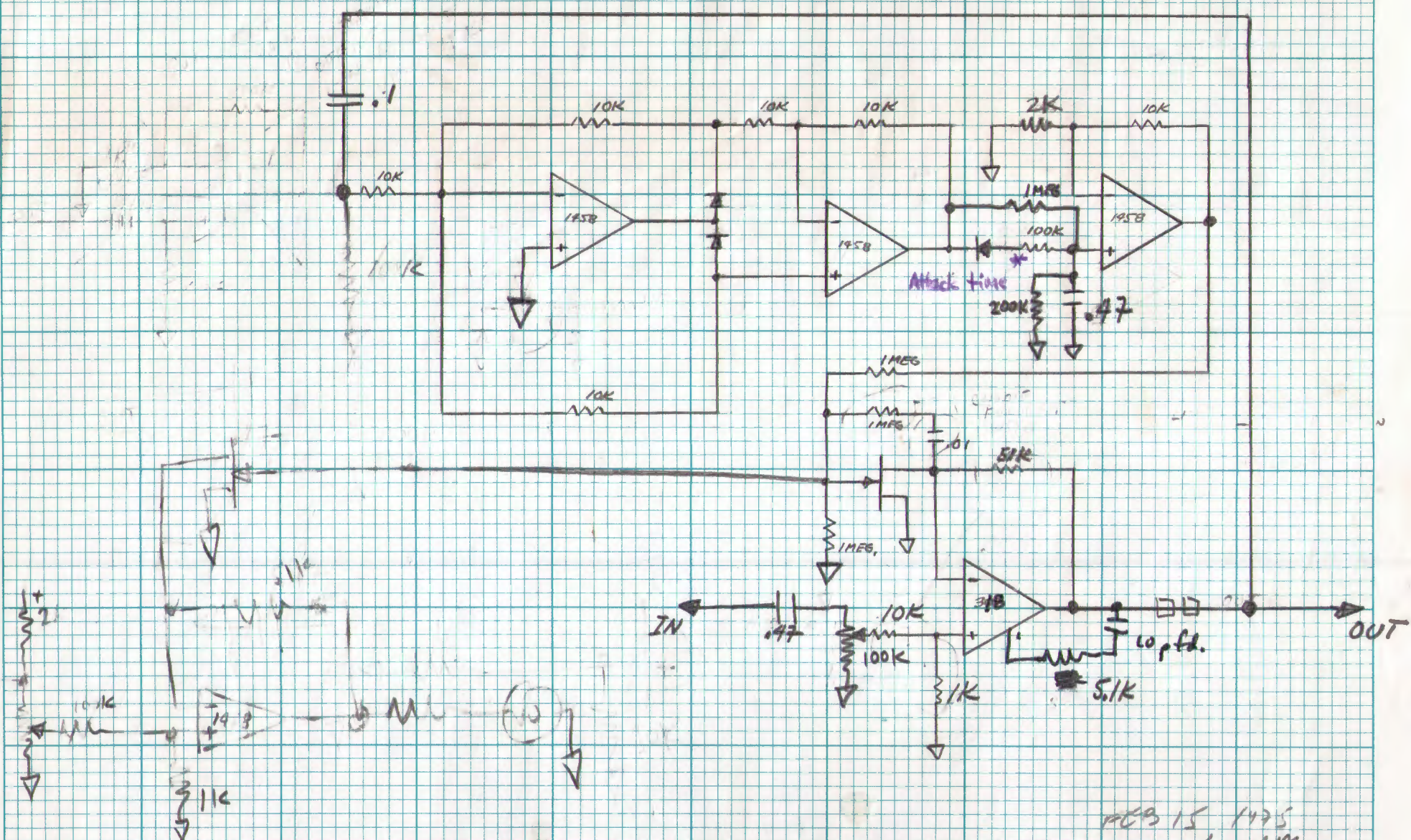

PEAK LIMITER AND EXP. COMPRESSOR
 REV. DAG DEC 2 1975


RES 15, 1475
 1475

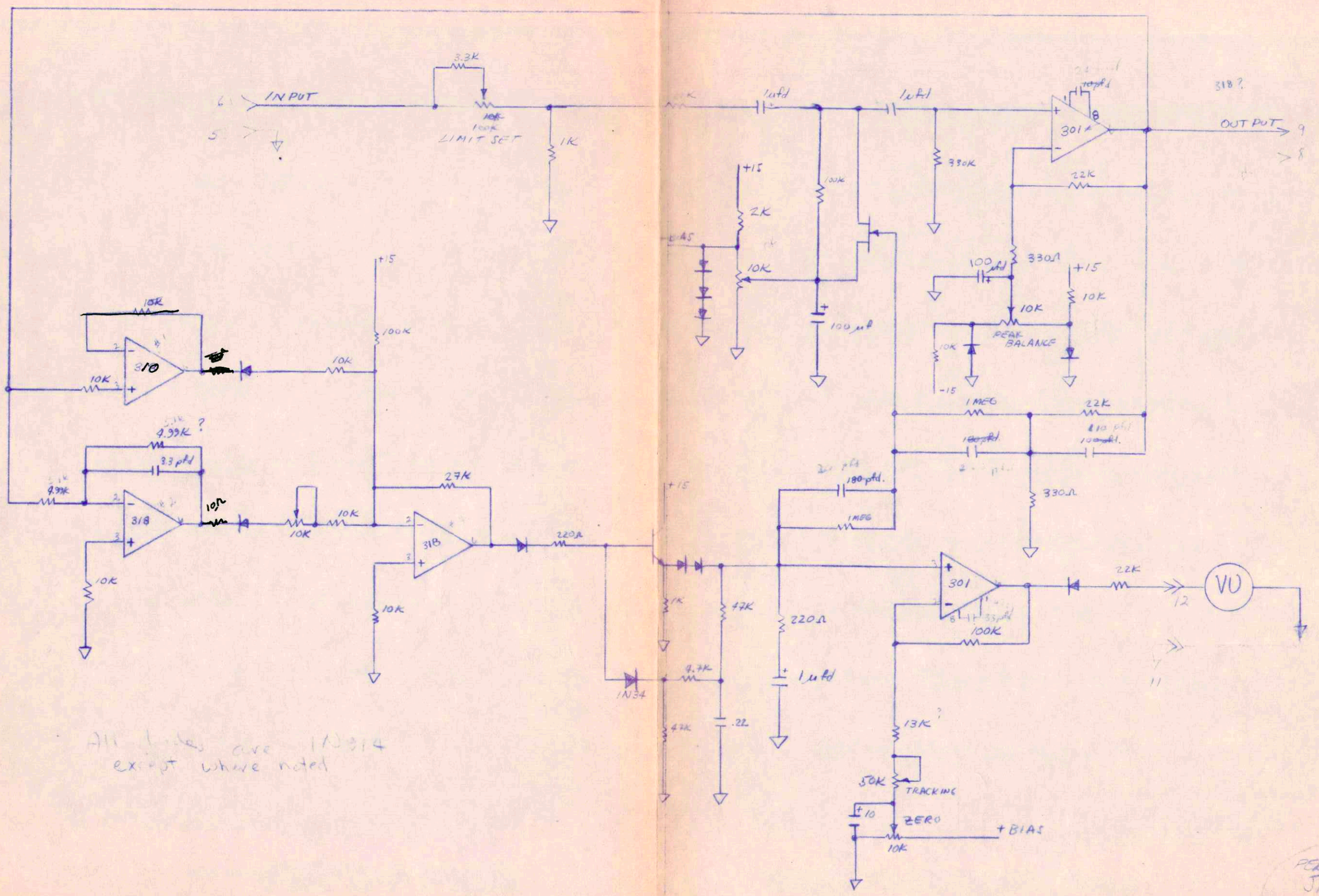

All diodes are 1N34
except where noted

PEAK LIMITED
JACK WILLIAMS
ATTN: RGD PAS

TYPE	REVISION	CODES	GEOMETRY	CASE
FD1780	Ø	DFN	DFN 2.5	TO-71
UNIT MARKING	FD1780	CUSTOMER	PACIFIC RECORDERS	
PACKAGE MARKING	FD1780	CUSTOMER DWG/SPEC NO.	REV.	BOTTOM LEAD CONFIGURATION

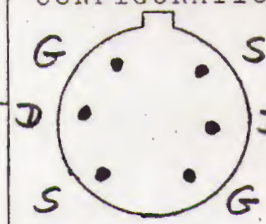

SPECIAL INSTRUCTIONS:

STATUS

Finding suitable FET's was not easy!!!

SEQUENCE	TEST SYMBOL	TEST TYPE	TEST CONDITIONS	PROD. LIMITS			CUST. LIMITS		
				MIN.	MAX.	UNIT	MIN.	MAX.	UNIT
1	IGSS	PC	V _{SG} = 15V, V _{DS} = 0		500	µA		1	nA
2	BVGSS	PC	I _G = 1µA, V _{DS} = 0	26		V	25		V
3	IDSS	PC	V _{DS} = 10V, V _{GS} = 0	4.5	14	mA	4.0	15	mA
4	V _p	PC	V _{DS} = 10V, I _D = 1µA		5.8	V		6.0	V
5	R _{DS}	P	V _{GS} = -1.5V, I _D = 100µA		1.9	KΩ		2.0	KΩ
6	R _{DS2}	P	V _{GS} = -1.0V, I _D = 1mA	310		Ω	300		Ω
7	1/R _{DS2}	P	" " " "	.82	1.0		.80	1.0	
8	C _{ISS}	Q	V _{DS} = 15V, V _{GS} = 0, f = 1MHz					8	pf

BASIC: 23 Mar 76

REVISION

PREPARED BY: *B Adkins*

APPROVED BY: PROD. EVAL. *GA*
 PROD. CONT. *GA*

Q.A.

REL.


COMPUTER

PAGE

of

3/15/76

SOLITRON DEVICES.

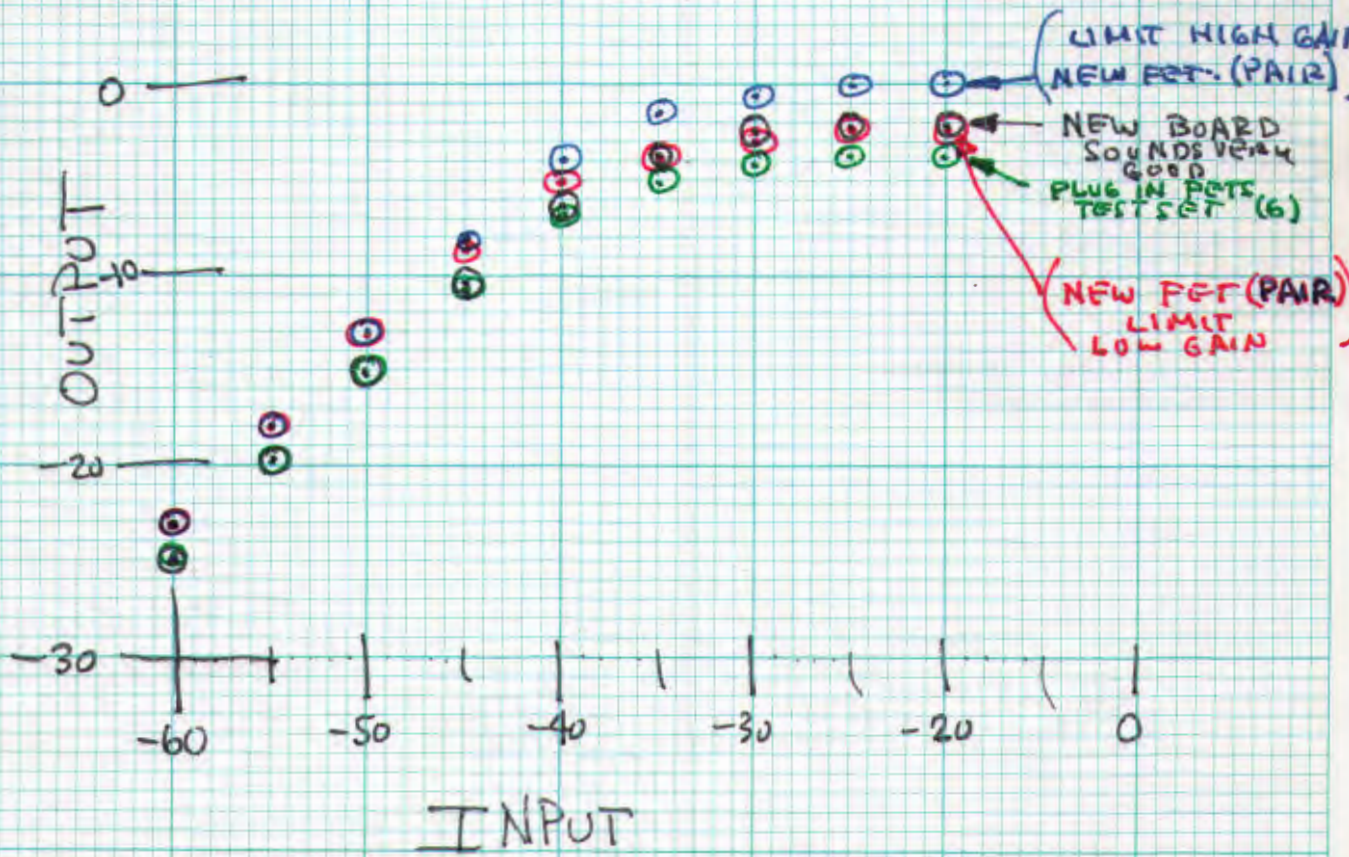

① IN34 - NO GAIN LAST STAGE
DIST. AT 6db 1%

② 14db gain
DIST @ 6db 0.4%

OUTPUT

10

0

-10

-20

-30

-40

INPUT

-60

-50

-40

-30

-20

-10


0


OLD
FET

0.4% dist

2K


60db
PUSH

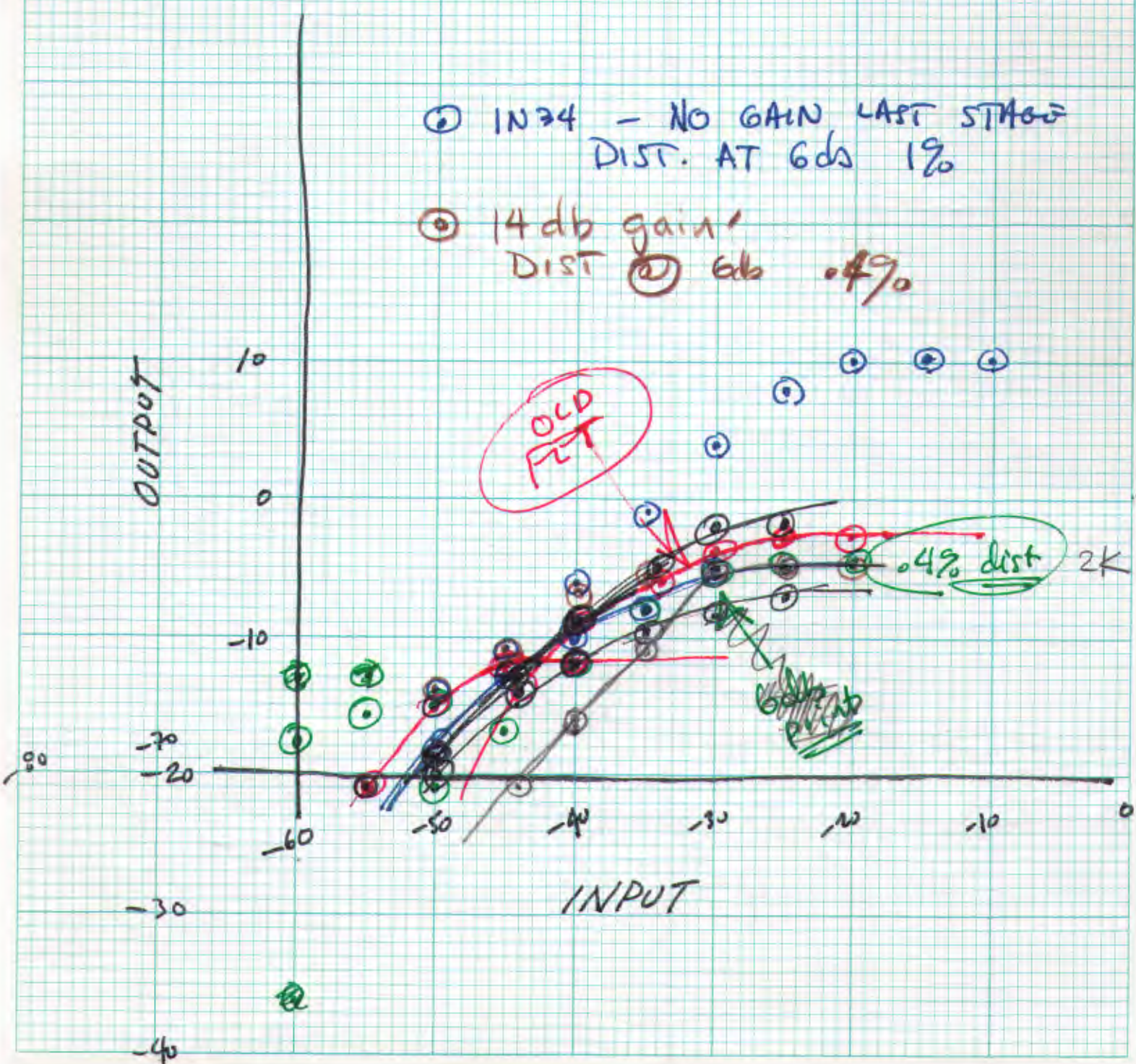

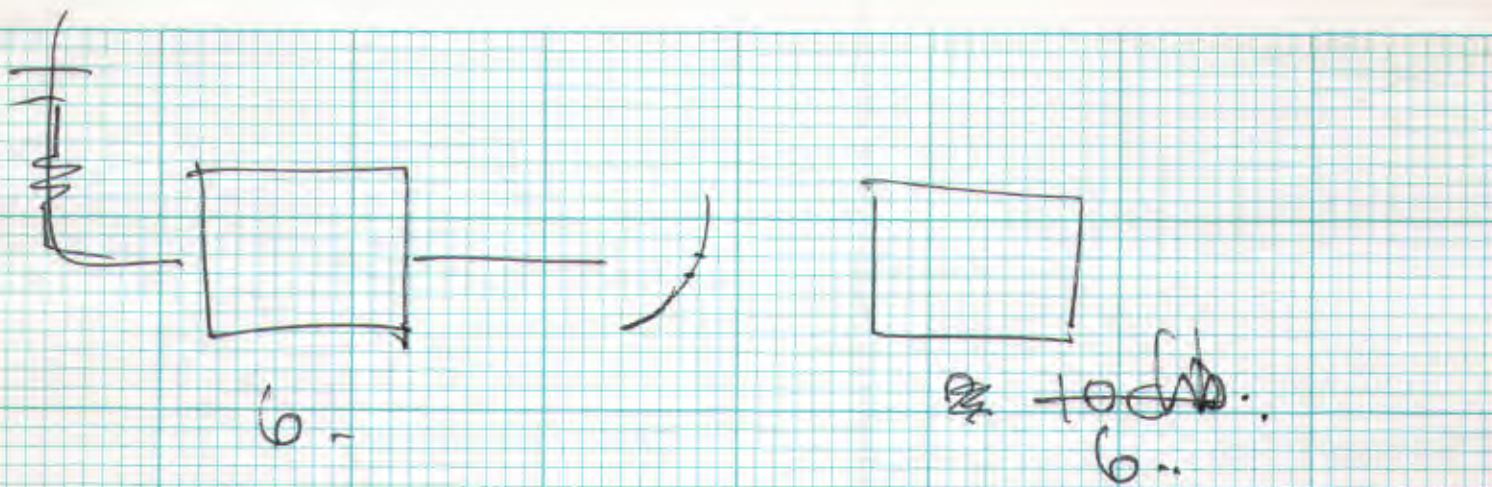


FAST LIMITER

⊙ old parameters IN34A.

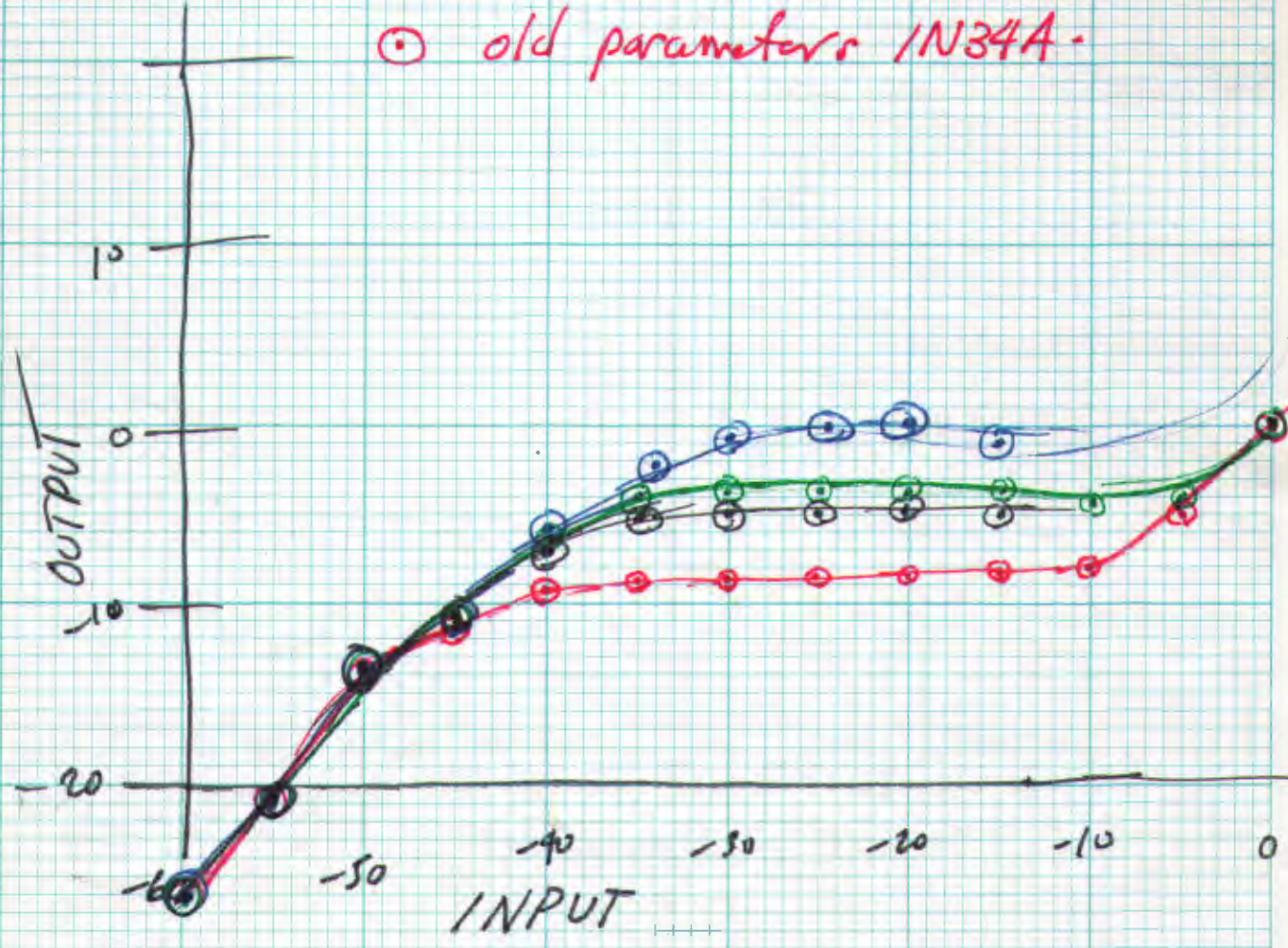

3/15/76
SOLUTION -

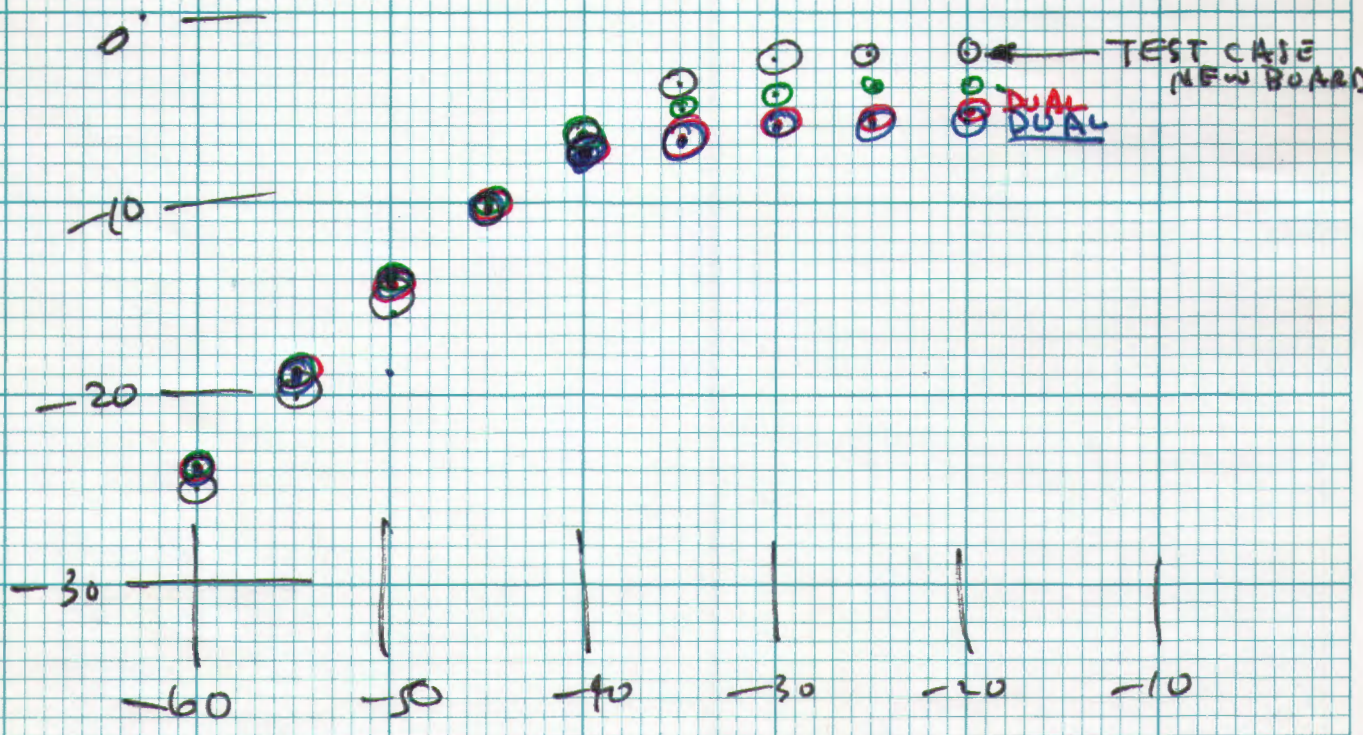


INFORMATION

SETUP

2/29/76

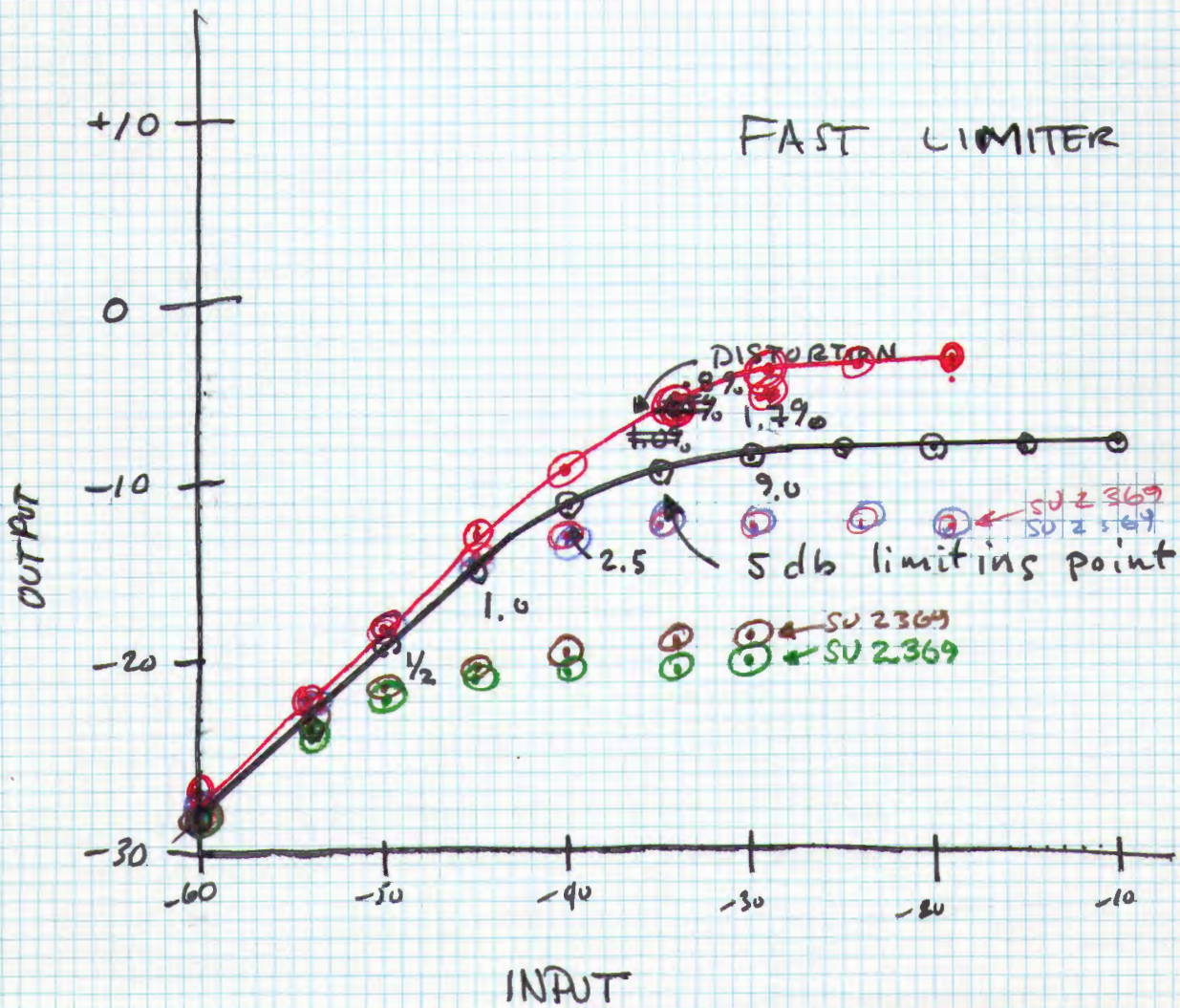GAIN FAST LIMITER *10 or 20db, 2N4303
 For 6db RMS is 5db Fast limiting
 Clipping level for 5db Fast
+6db
 All Tests 1KHz



FM TOTAL GAIN 50db S/N Full gain: input -30
 66db.

AM Broadcast, Signal Processing

The signal chain in audio broadcasting is "Capacitor", or "Transformer" Coupled
The D.C. component is not present (Unlike NTSC Video Modulators)

The AC signal has its zero reference the Average signal value
However complex audio signals are often asymmetrical, that is the
peaks on one side are greater than the other...

This characteristic is often associated with a particular musical instrument or Person's Voice


AM broadcasting has the general Modulation equation of Carrier-Modulation (Both AC Signals)
It is not Possible to have Negative Peaks... Broadcasted signal would clip,
causing severe (and illegal) 'splatter', spurious signals
However the positive peaks are allowed to be 125% of the carrier signal

So it is desirable to match the Audio Signal positive peak Asymmetry as Positive Modulation
So an Automatic Polarity Switch is employed...

To avoid a discernible artifact, switching takes place during a lull in the programming material


The final step, somewhere downstream, is the Clip the result...
to assure compliance, even if the the phase is wrong!

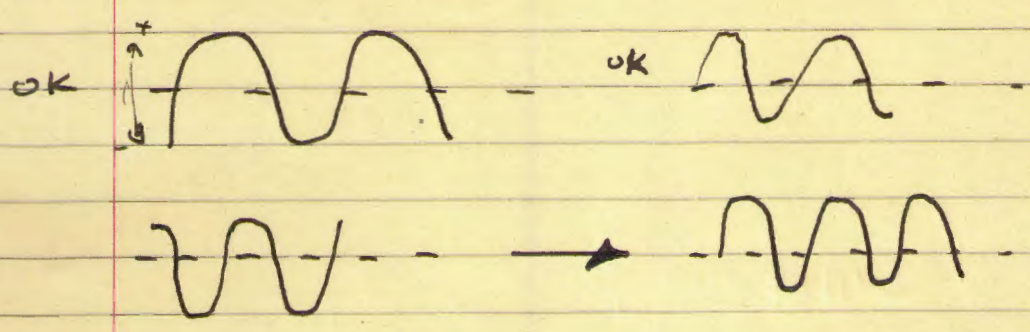Problem: provide automatic polarity switching of signal to provide asymmetrical swing with high peak positive ...




Notice this is not a level shift, but a polarity reversal!

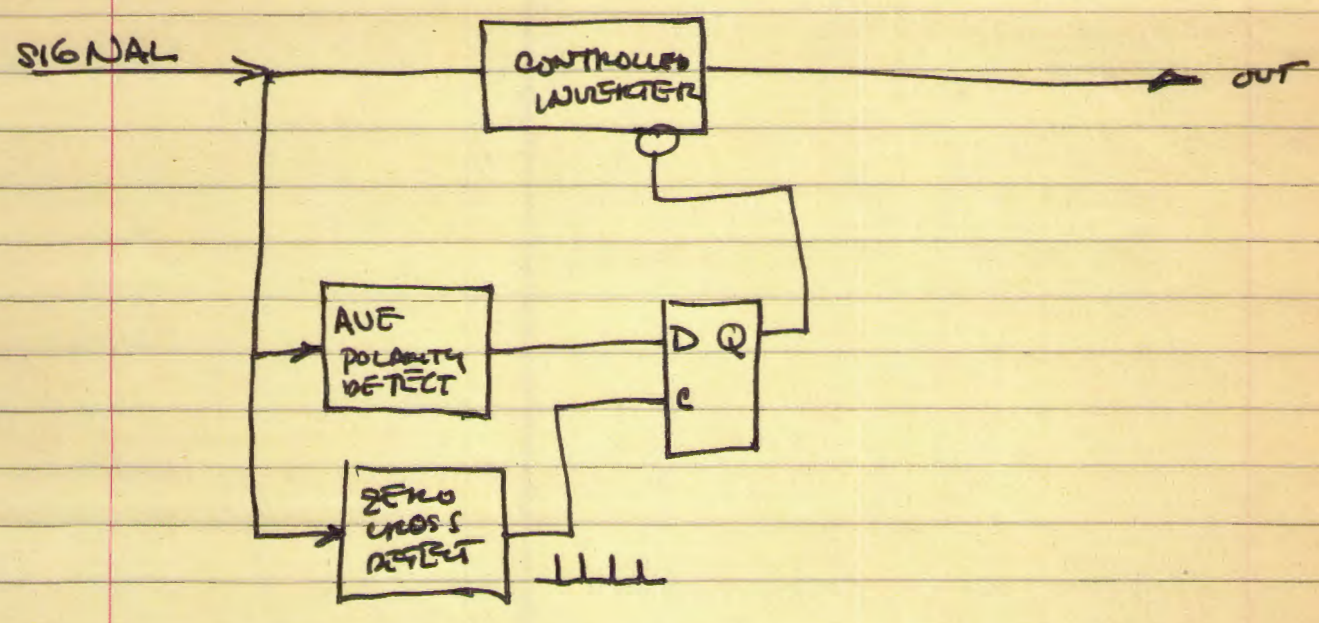
Reversal must be accomplished on a zero crossing




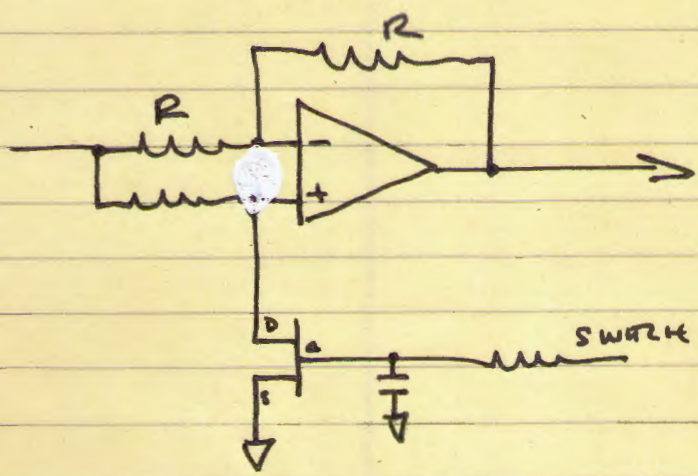
Simple realization of controlled inverter -




Simple polarity analyzer

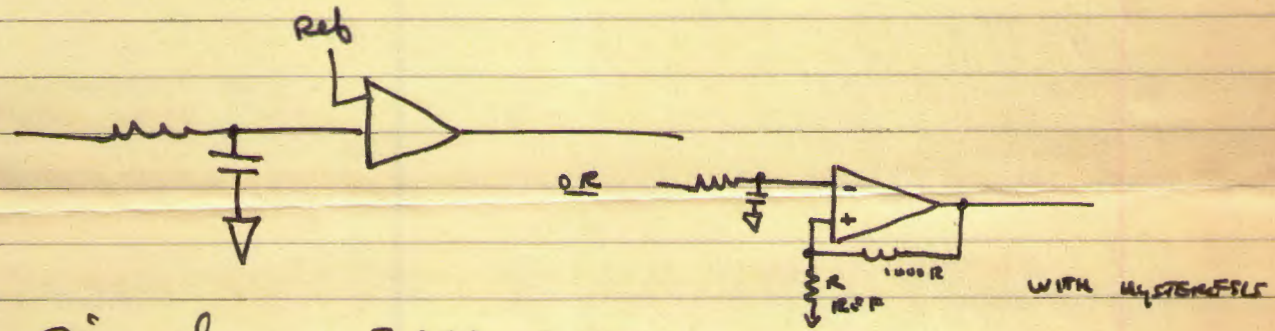

Simple zero cross

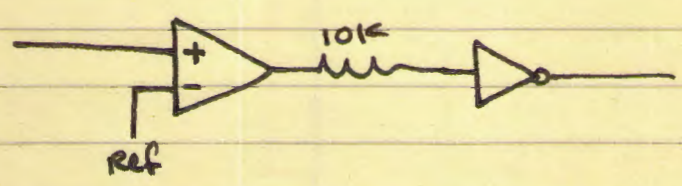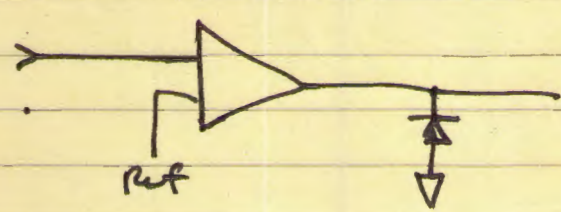


OR

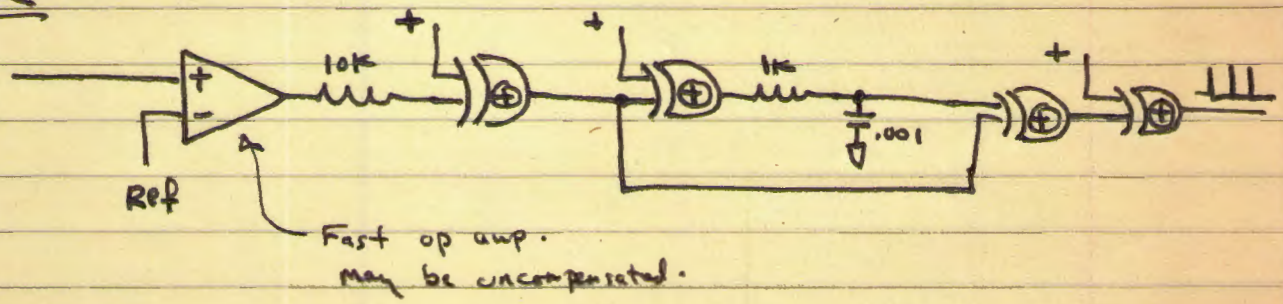

Fast op amp. May be uncompensated.


Redo of inverting amp

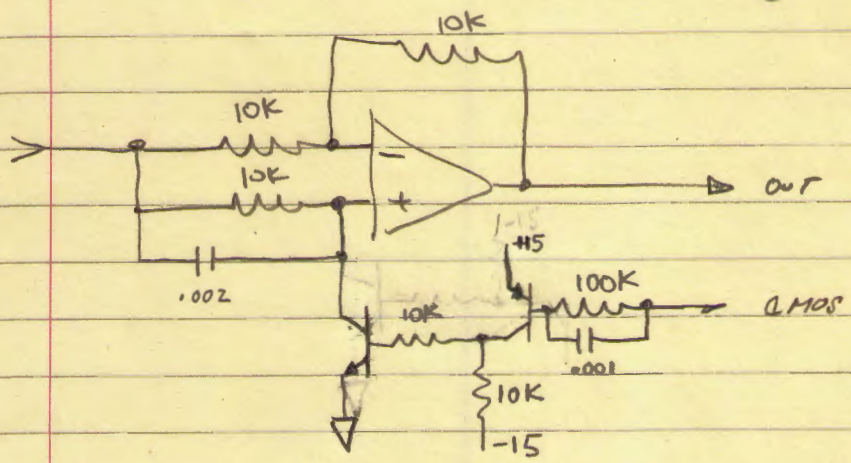


less than .005 volts offset

Now we need a circuit to determine which peaks are higher... neg or pos.

we could use ...

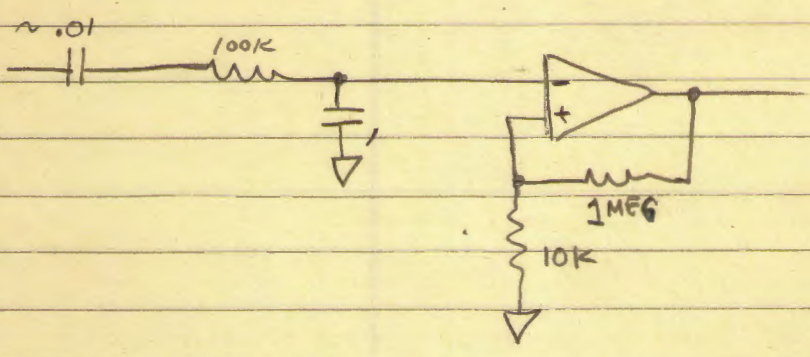

However circuit

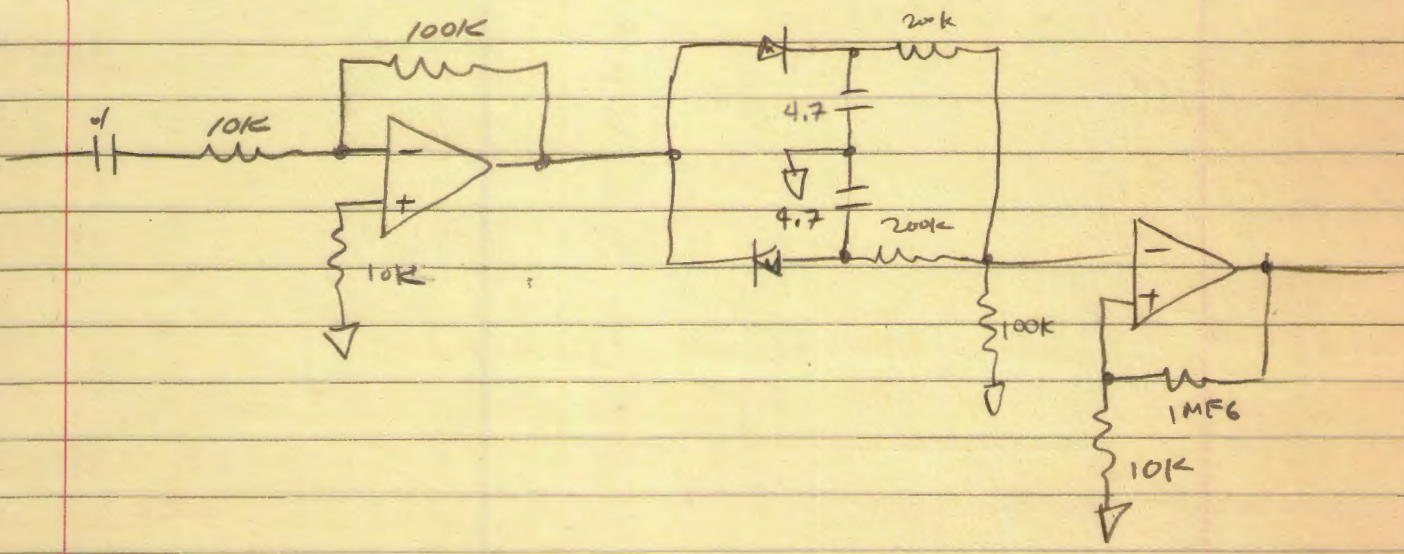


January 27 -

The thing sounds like a ping-pong match.

I must only allow phase reversal - during a quiet time - need a lull detector.

Try

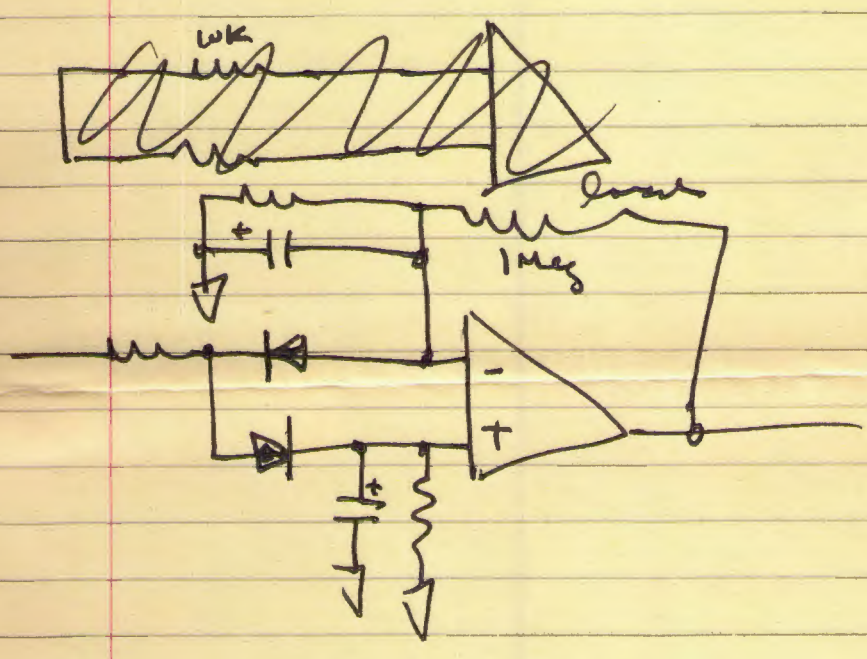


If signal below diode threshold output goes to ground. (see 1 meg?)

If signal either pos or neg above threshold ~~no~~ out. signal goes high.

See Rev. Jan 28 - works very well.

Suggest circuit changes - and things to try...

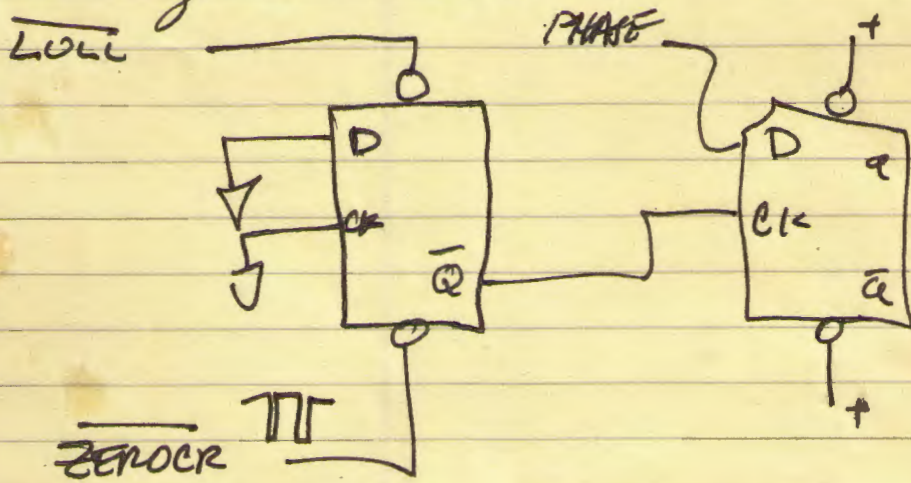
Logic for "anding" Lull detect, and zero cross




This circuit uses property of 7474 - such that when both clear and preset are low both output are high.

Then we need exclusive nor gate - or equiv.

May be obtained from 7402 Nor gate -

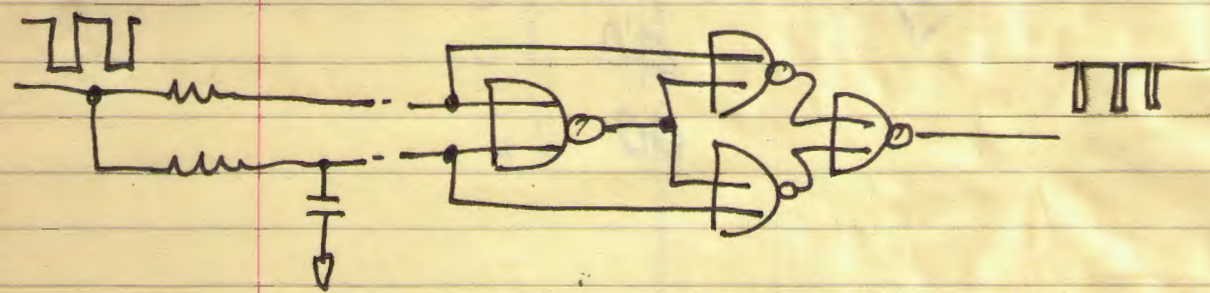


OR we might use another 301

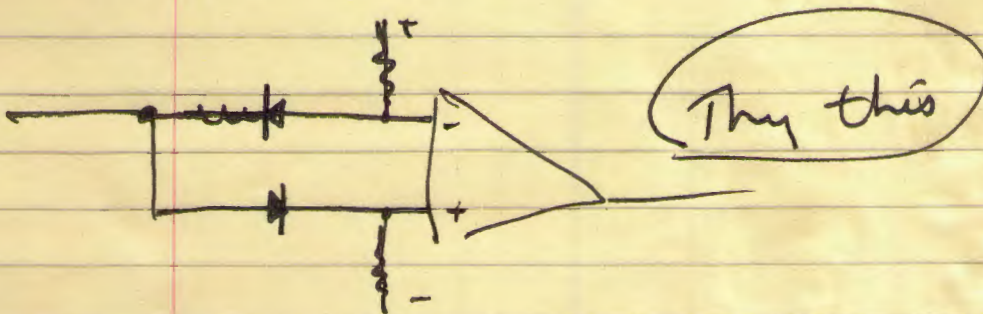

A small amount of noise is attributable to dc offset switching.

- solution use - blocking cap. input -

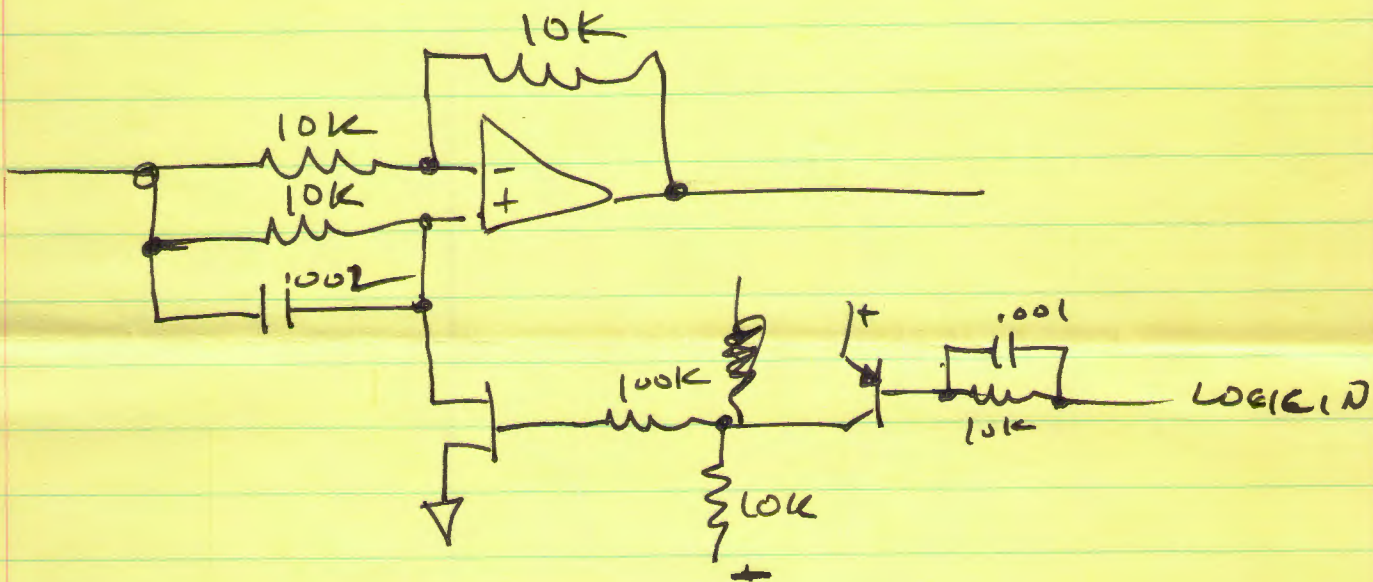
also overshoot - in sudden positive input -
solution shunt capacitor on input to new circuit



Might - all also try no zero cross detection circuit - just hull -

It would seem that the "pop" when switching this can be improved by slowing the phase switching time - a tradeoff between distortion and pop is achieved -

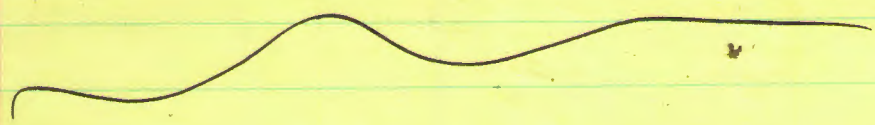notice also if we use this tradeoff - zero cross detection is superfluous



AUTOMATIC POLARITY (WITH ZERO CROSS SWITCHING)

RA GRAY JAN 25, 1975


REV. JAN 28 - LULL DETECT.

(REV FEB 5.

REV. JAN 30.

REV FEB 4

PRELIMINARY

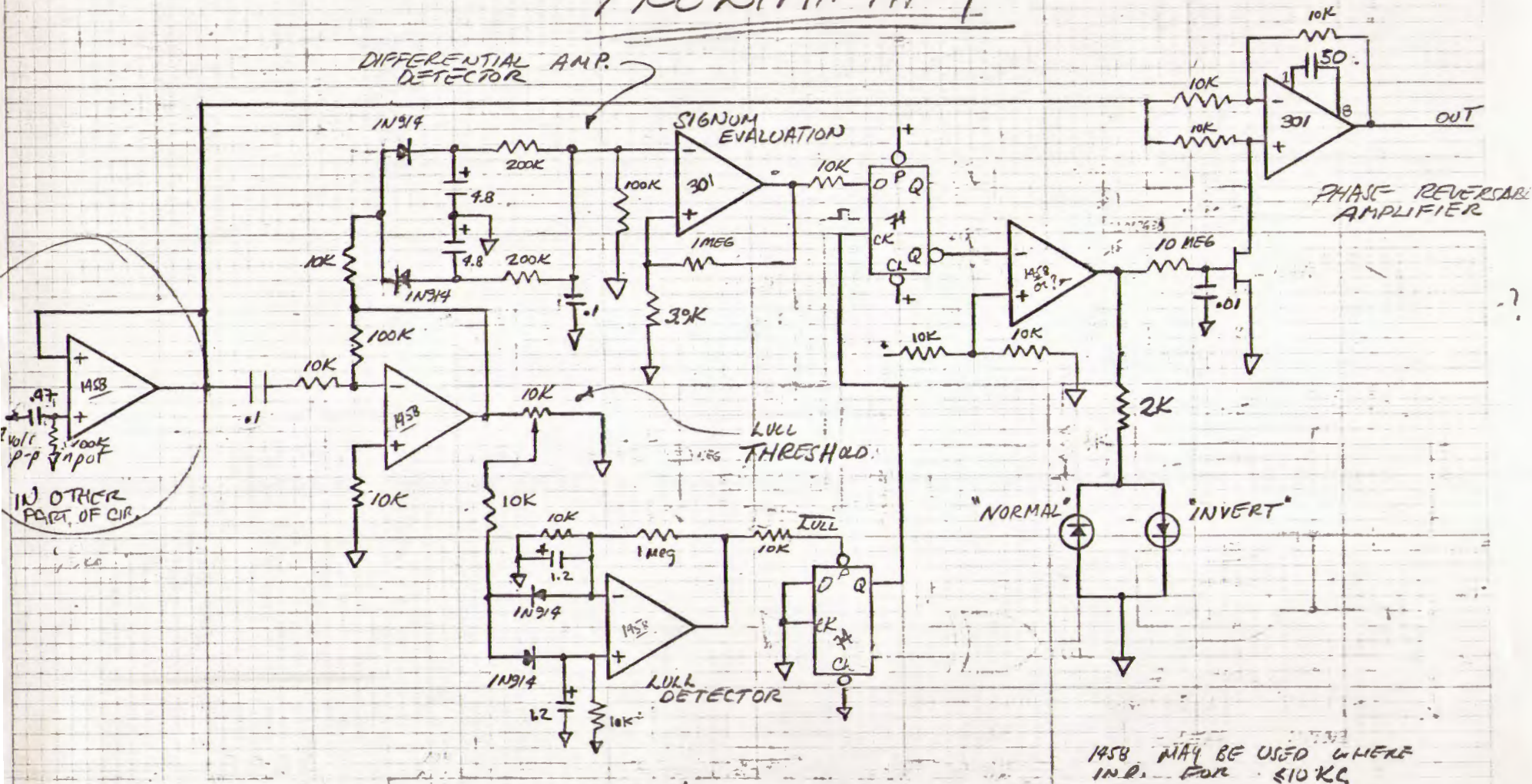


AUTOMATIC POLARITY (WITH ZERO CROSS SWITCHING)

RA GRAY JAN 25, 1975 REV. JAN 28 - LULL DETECT.

REV. JAN 30

PRELIMINARY

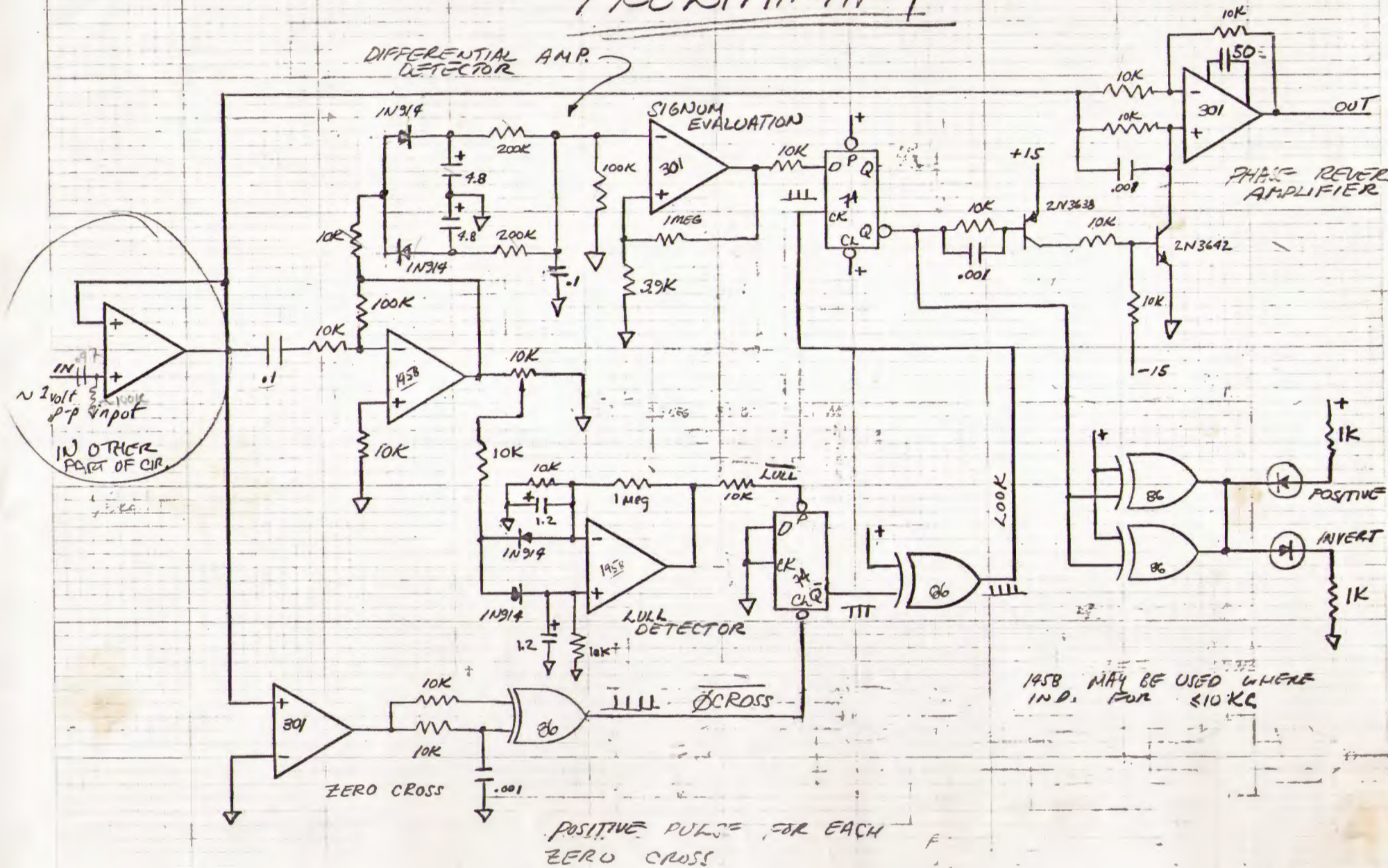


AUTOMATIC POLARITY (WITH ZERO CROSS SWITCHING)




RA GRAY JAN 25, 1970 REV. JAN 29 - LULL DETECT.

REV FEB 5. REV. JAN 30.
REV FEB 4

PRELIMINARY

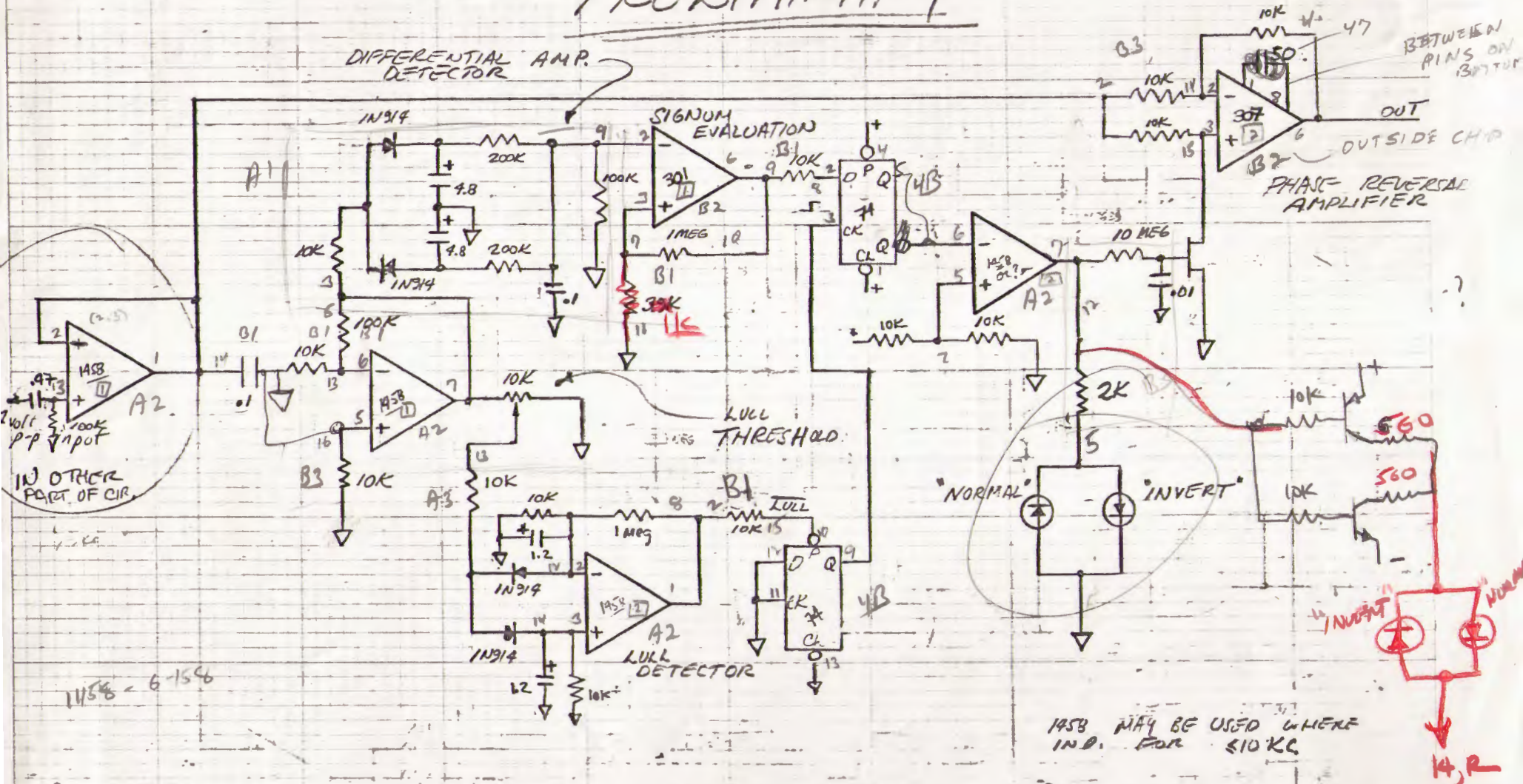

Repeated here for clarity

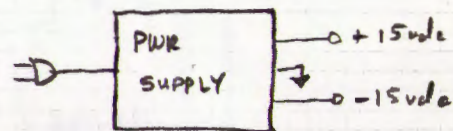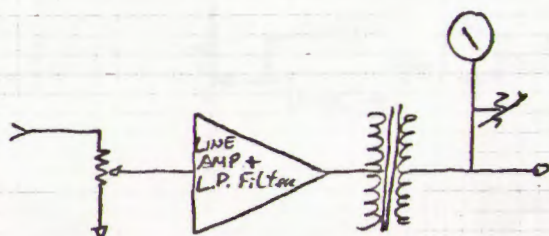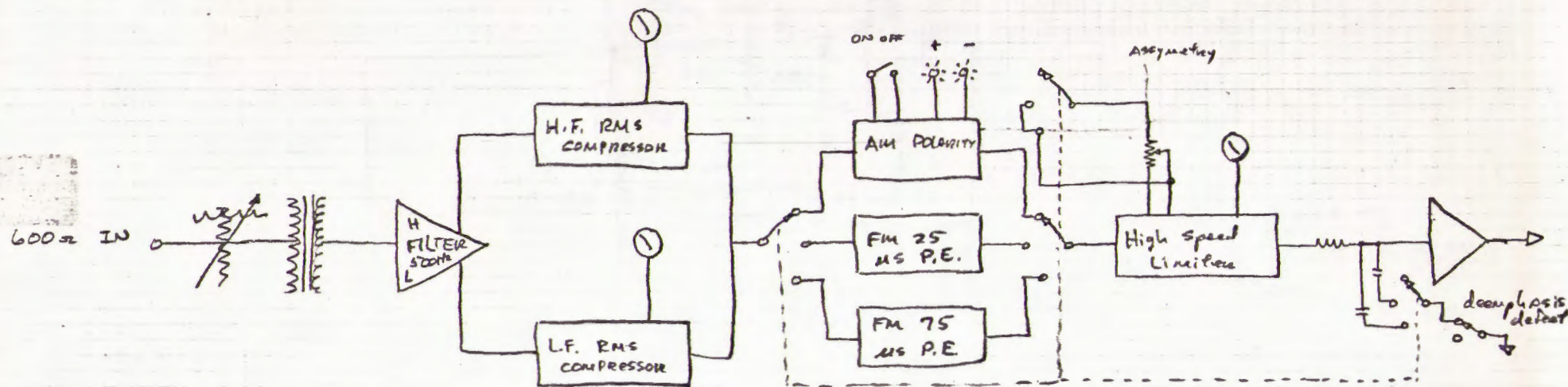

AUTOMATIC POLARITY (WITH ZERO CROSS SWITCHING)

RAT GRAY JAN. 20, 1975

REV. JAN 28 - LULL DETECT.


REV FEB 5.

REV. JAN 30.

REV. FEB 9

REV FEB 4

PRELIMINARY

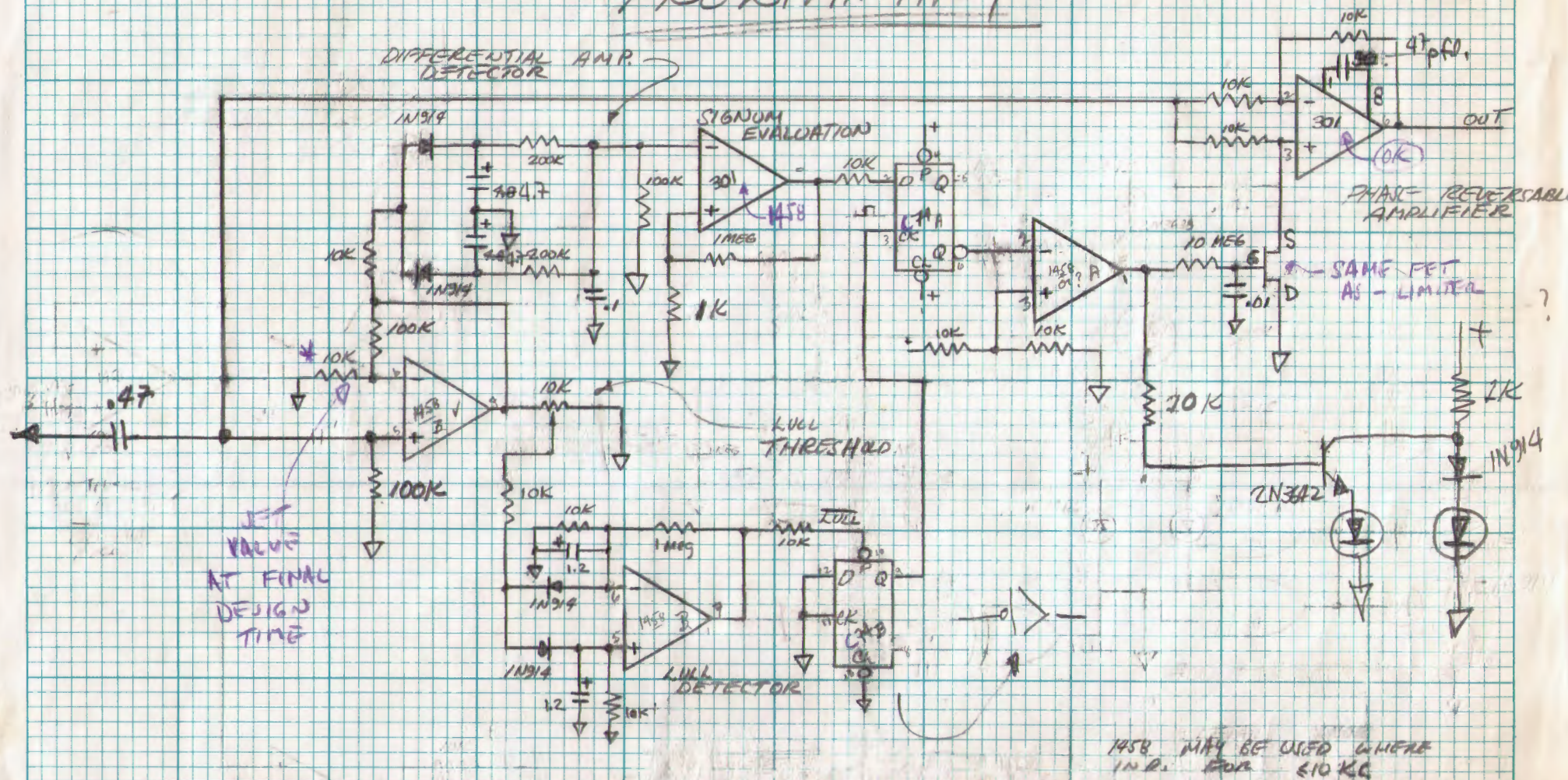


AUTOMATIC POLARITY (WITH ZERO CROSS SWITCHING)

RA'GRAY JAN. 25, 1975 REV. JAN 28 - LULL DETECT.

UNOPTIMIZED

PRELIMINARY

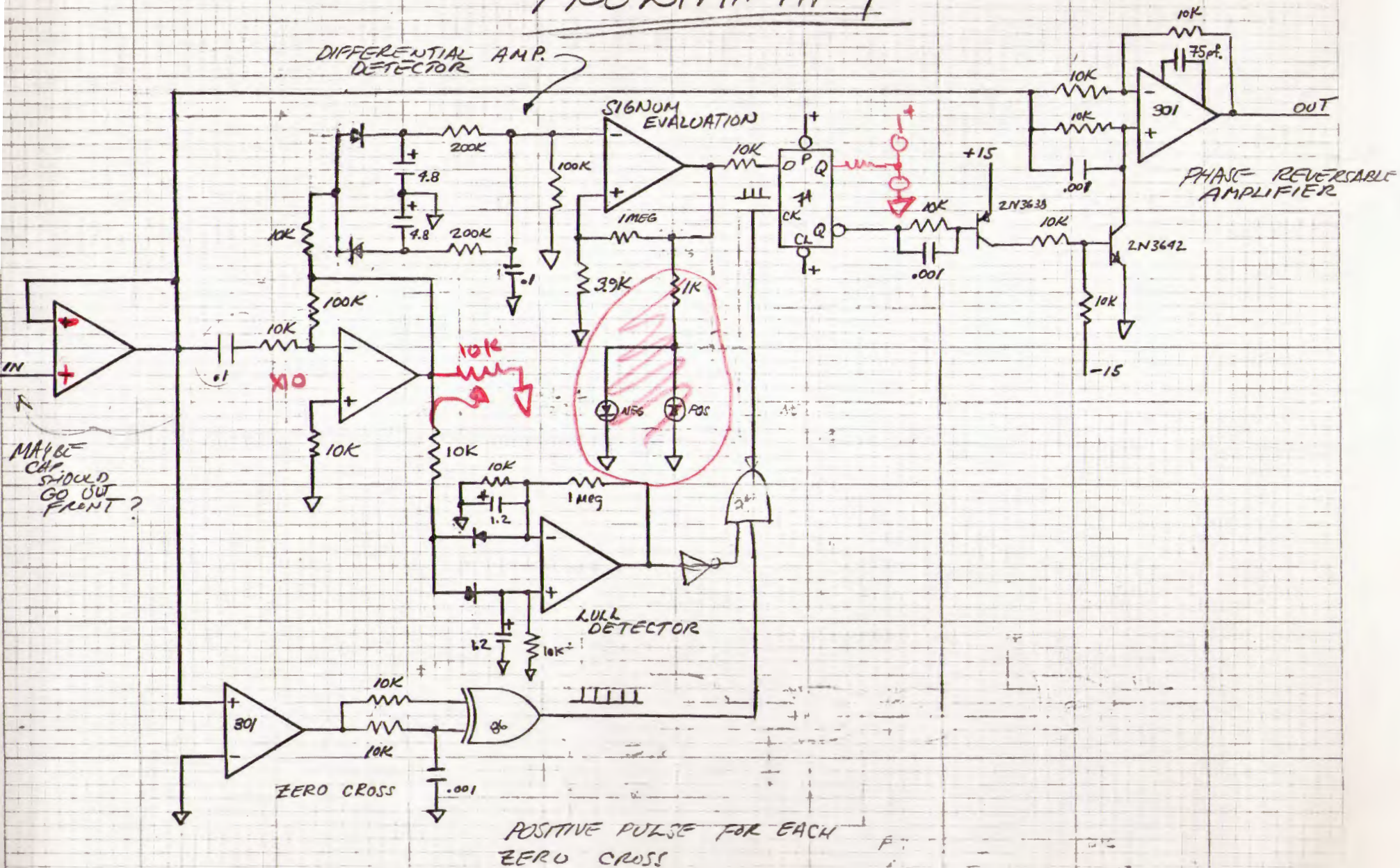

FM Broadcast, Signal Processing

FM Audio Signals are "Pre-Emphasis", high frequencies accentuated before transmission
And de-emphasized in the Radio Receiver

To assure the Audio Signal is Properly Limited at the transmitter
It is necessary to pre-emphasize, in MultiLimiter, do signal processing
And then return the signal to 'normal' audio for the transmitter
(And option could be to not Pre-emphasize in the Transmitter, and not de-emphasize in the Limiter)



Several Pre-emphasis standards are supported:

None


25uS, for Dolby "B" Systems??? (Never adopted as a Standard)

75uS, U.S., Standard Broadcast Channel(s), U.S. NTSC Television Audio

Extremely simple Brute Force circuit!!!

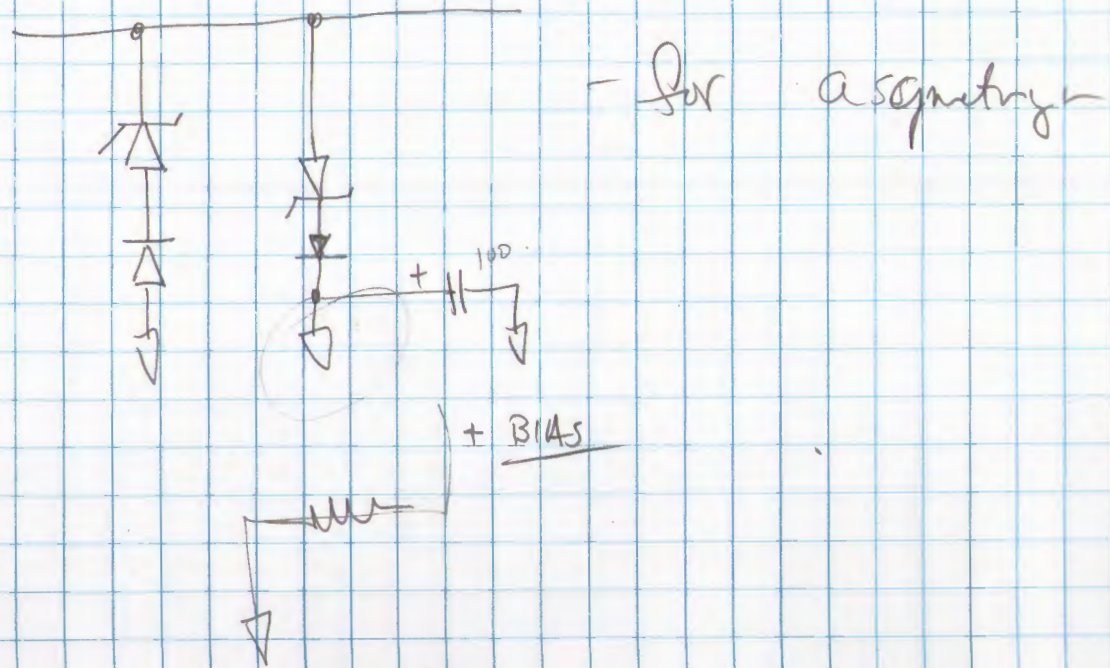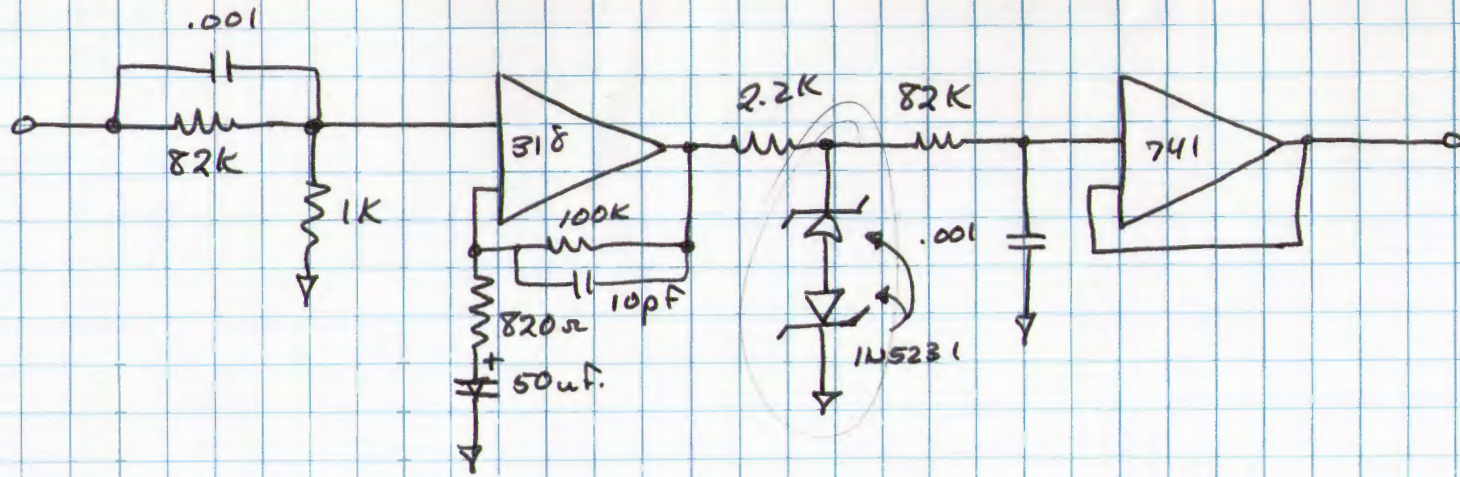

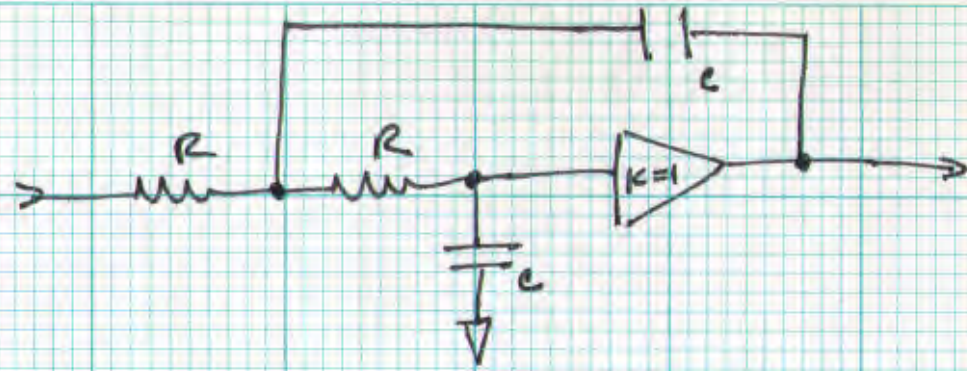Low Pass filter,
Remove audio that should
not be processed



for 15Kc or 9.42×10^4 rad/sec

$$\omega_0 = \frac{1}{RC} \quad \text{choose } c = .001 \mu\text{fd.}$$

$$\text{then } R = \frac{1}{.001 \times 10^{-6} * 9.42 \times 10^4} = \sim 10K\Omega$$

for 10KΩ $\sim 15.9 \text{ Kc}$



choose .0011 μfd.

10K and .0011 μfd - we have 14.5Kc
ok - ?

$$R = \frac{1}{.0022 \times 10^{-6} * 9.42 \times 10^4} = 4.83K -$$

OR For 4.7K
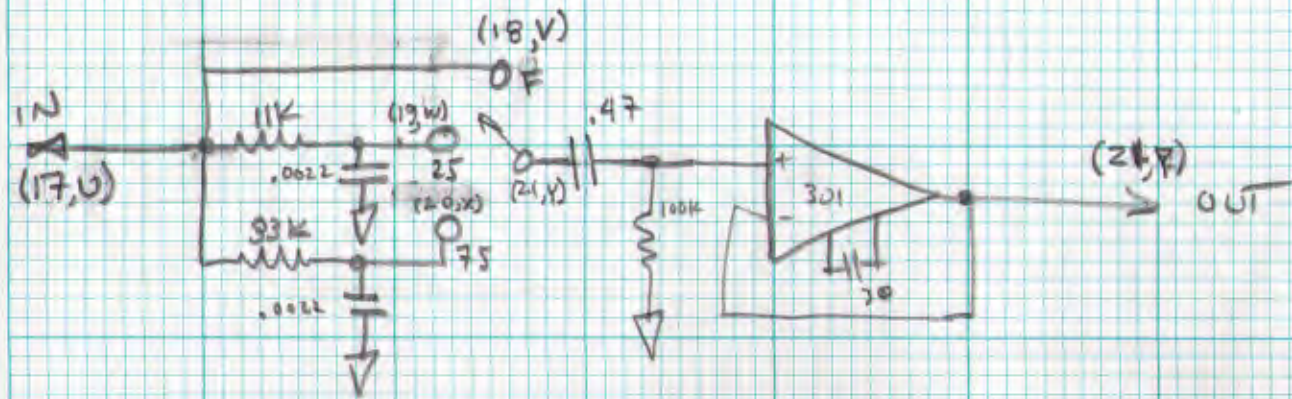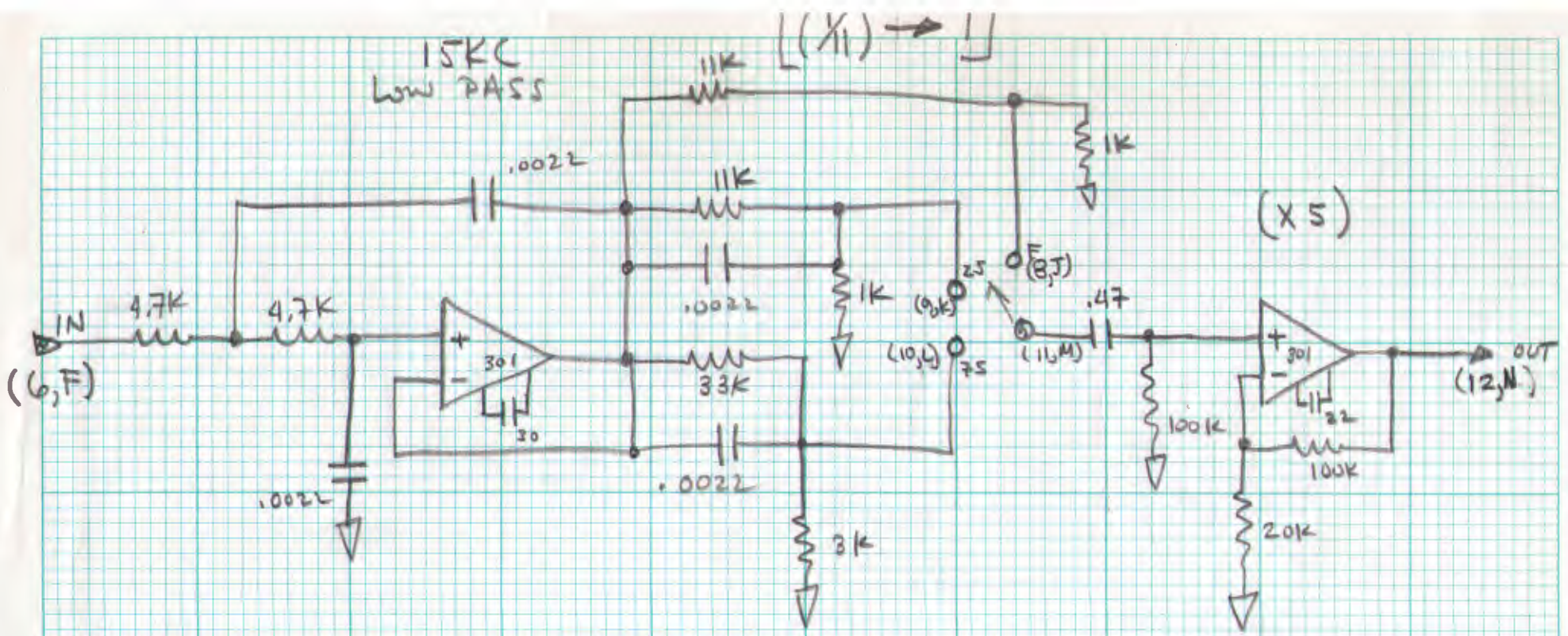
$$\omega_0 = \frac{1}{.0022 \times 10^{-6} * 4.7K} = \underline{15.4 \text{ Kc}}$$




MULTIMETER

SWITCHABLE EMPHASIS -

PA 6PA


3/16/75

15Kc low pass

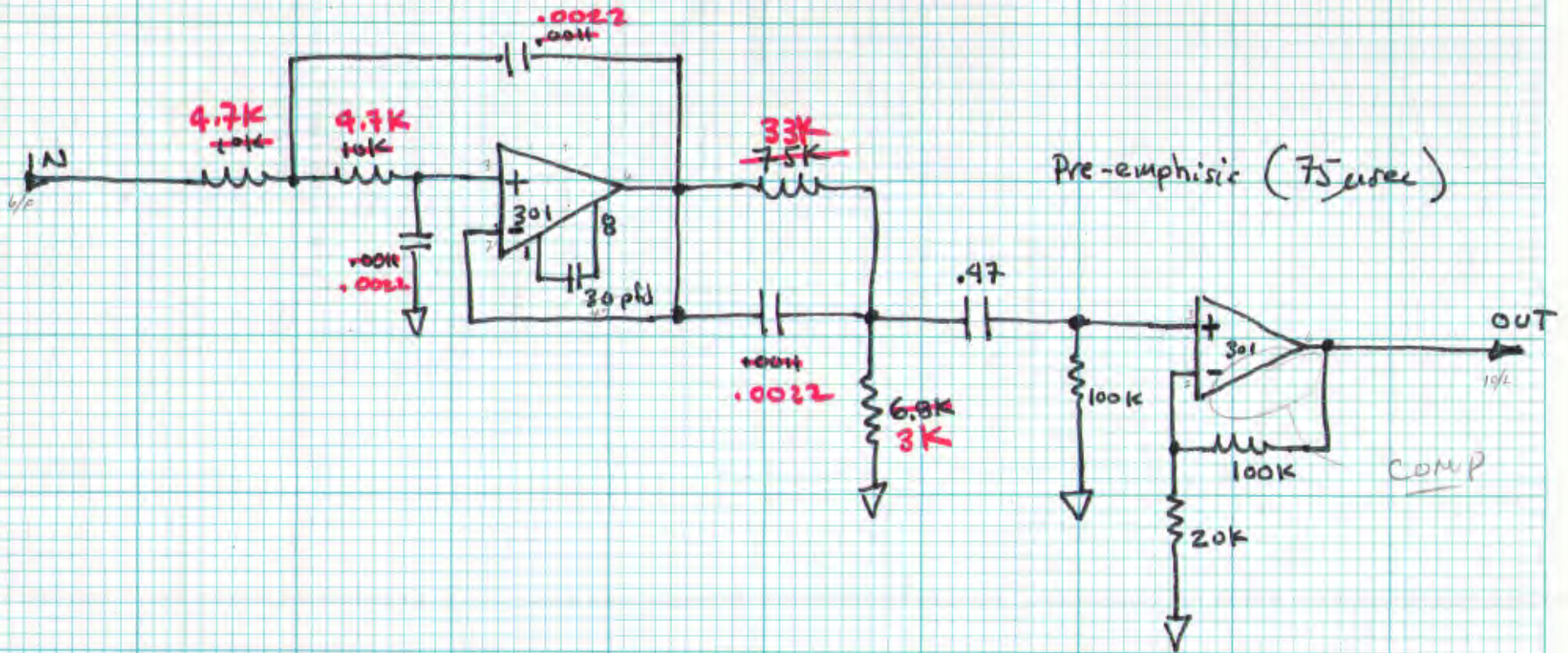


Pre-emphasis (75 usec)

De-emphasis

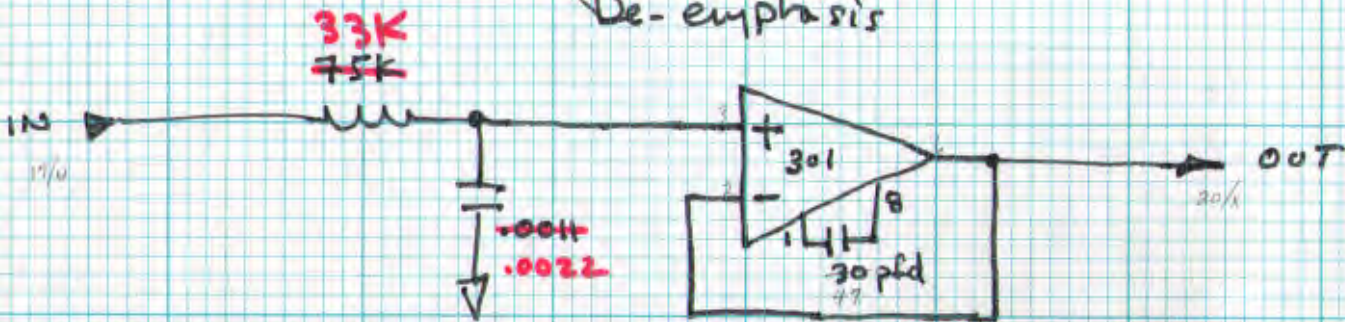

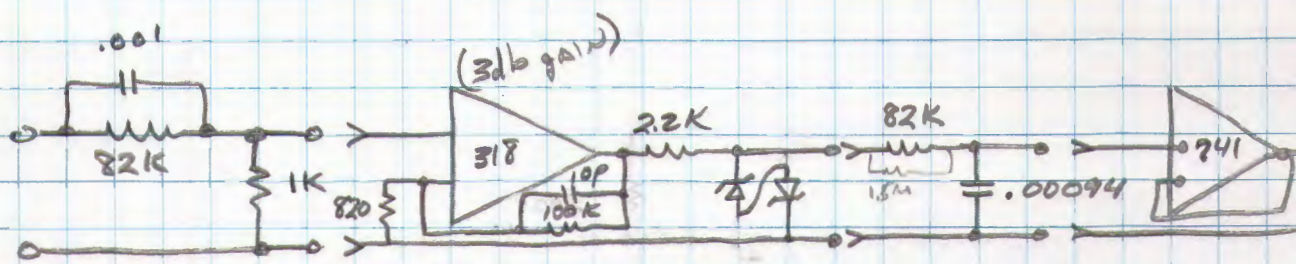Multimeter
pre emphasis
de emphasis
for FM
PGA Gmty
3/10/75





	<u>circuit</u>	<u>75 us sfd</u>	<u>AMP</u>	<u>circuit</u>	<u>AMP</u>
100 Hz	0	0	0	0	0
200 Hz	0	.05			
300 Hz	0				
400 Hz	.1	.2			
500 Hz	.2				
600 Hz	.4				
700 Hz	.5	0.5			
800 Hz	.6				
900 Hz	.8				
1 KHz	.95	.9	0	0	0
1.5 KHz	1.9			0	
2 KHz	3	2.8		-.05	
2.5 KHz	4			-.1	
3 KHz	5	4.8		-.1	
3.5 KHz	5.9			-.15	
4 KHz	6.7			-.15	
4.5 KHz	7.5			-.15	
5 KHz	8.3	8.2	0	-.2	
5.5 KHz	9			-.2	
6 KHz	9.6			-.2	
6.5 KHz	10.3			-.25	
7 KHz	10.8	11.4		-.25	-.1
8 KHz	11.9			-.3	
9 KHz	12.7			-.3	
10 KHz	13.6	13.7	0	-.3	-.2
11 KHz	14.4			-.35	1
12 KHz	15			-.35	-.25
13 KHz	15.8			-.4	1
14 KHz	16.4			-.4	-.3
15 KHz	17	17.1	0	-.4	1
16 KHz	17.6		0	-.45	-.3
17 KHz	18.2		0	-.45	
18 KHz	18.6		0	-.45	
19 KHz	19.1		-.05	-.5	
20 KHz	19.5		-.1	-.5	-.3

The Wire wrap Version for NAB 1975
The Input High Pass filter is not shown


Some drawings are shown previously in this section

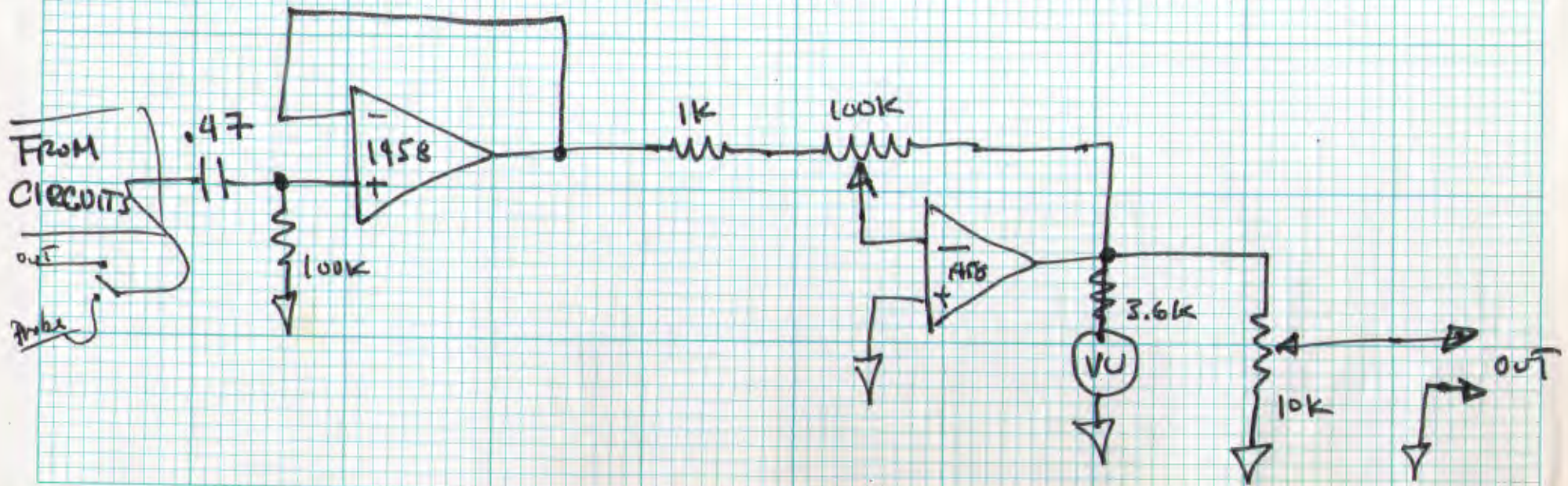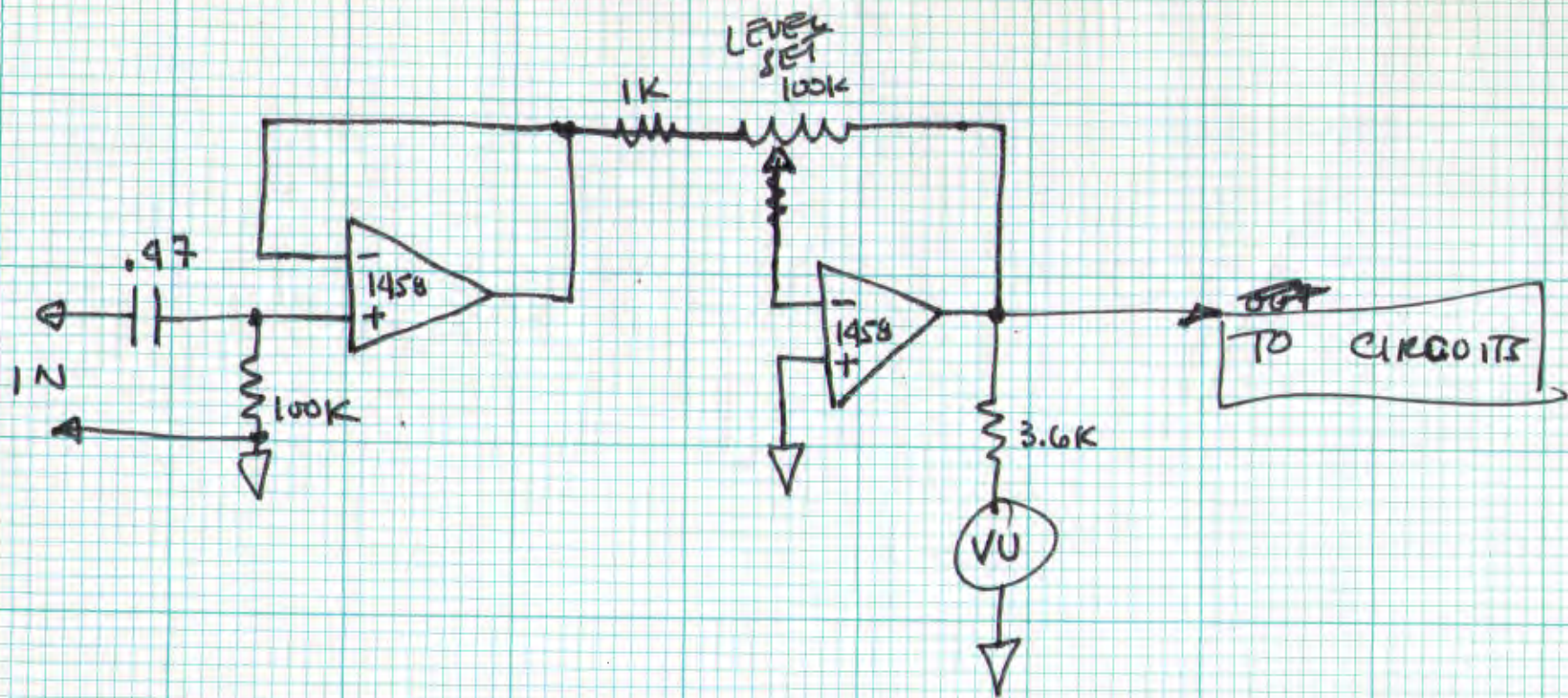The NAB Model, had no Fancy Input or Output Sections!!!



FILTER

INPUT

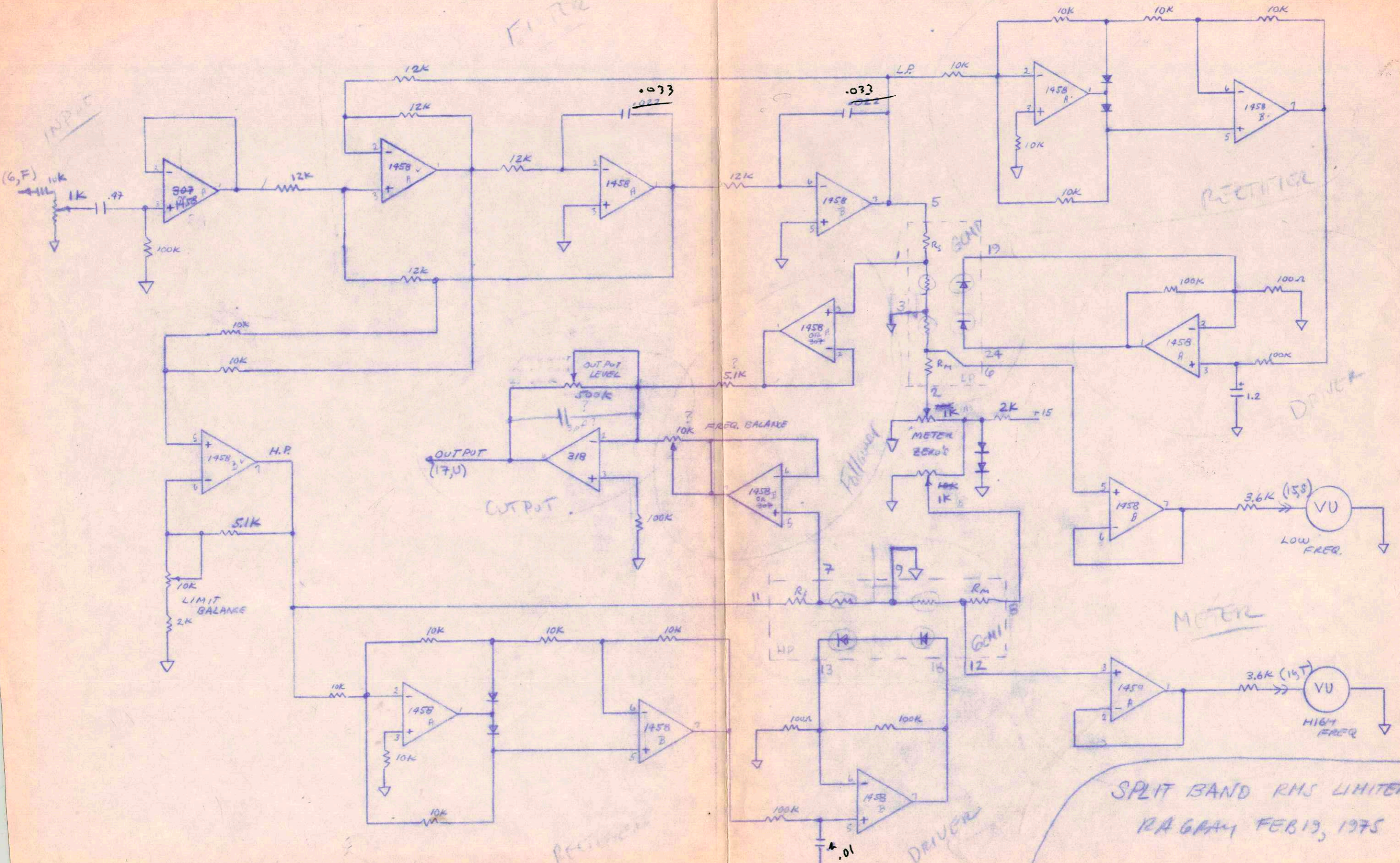

RECTIFIER

DRIVER

METER

OUTPUT

OUTPUT (17,0)

SPLIT BAND RMS LIMITER

RA GAN FEB 13, 1975

RECTIFIER

DRIVER

FOLLOWER

GEN

30M

LP

HP

.01

0.033

0.033

5.1K

10K

100K

10K

10K

10K

10K

10K

12K

12K

12K


12K

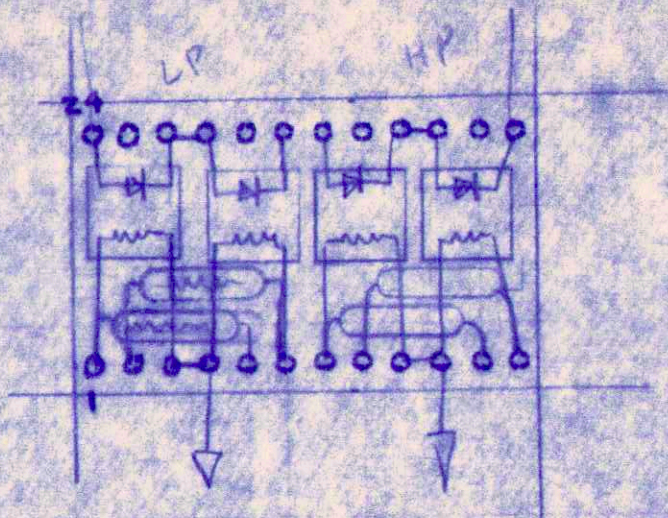

2x

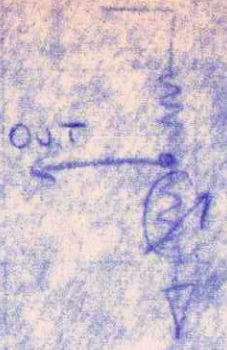


1000
1000
1000

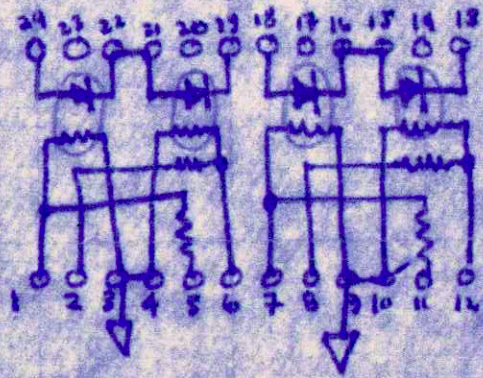

MULTIMETER



GAIN CONTROL MODULE
(GCM)
LAYOUT

PAGRAY 8/12/74

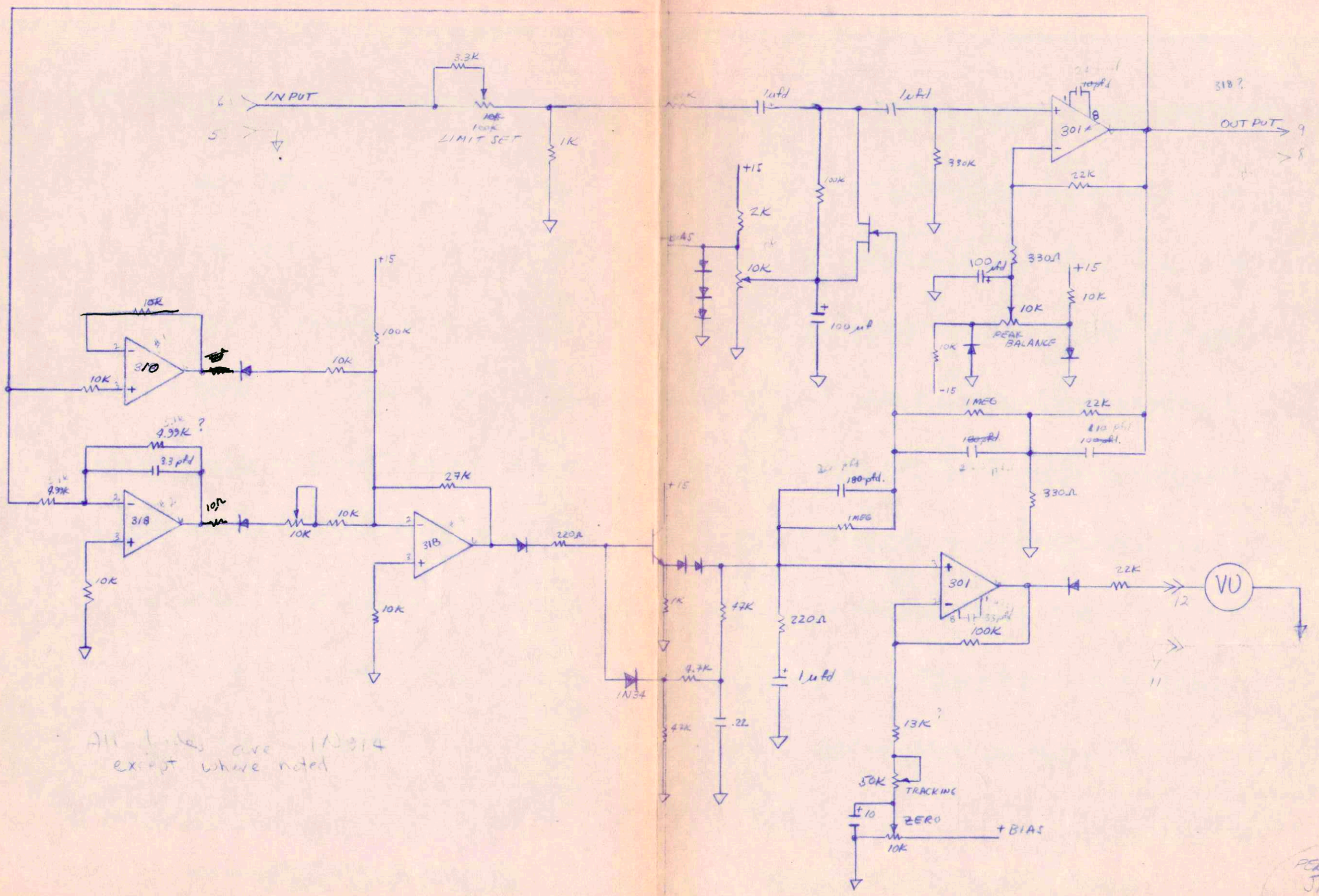

All diodes are 1N34
except where noted

PEAK LIMITED
JACK WILLIAMS
ATTN: RGD PAS

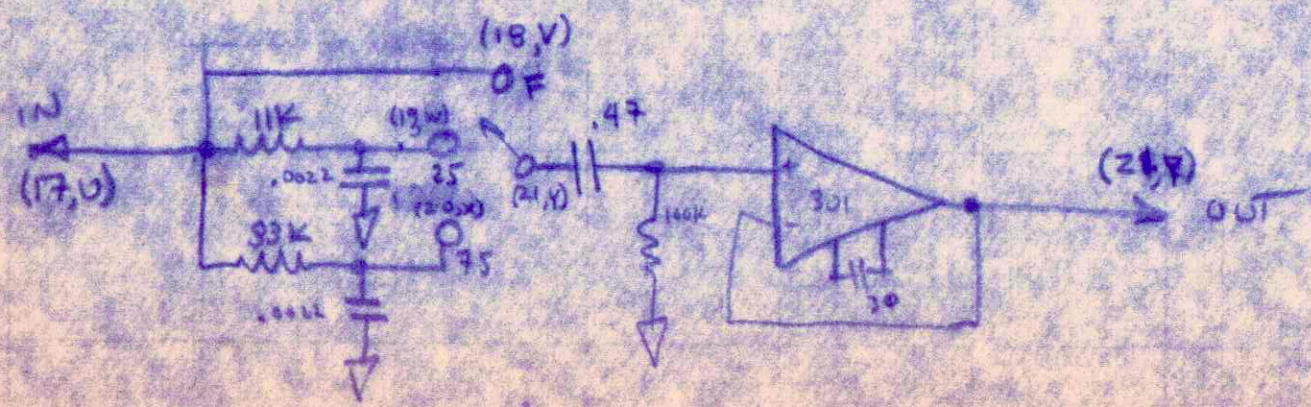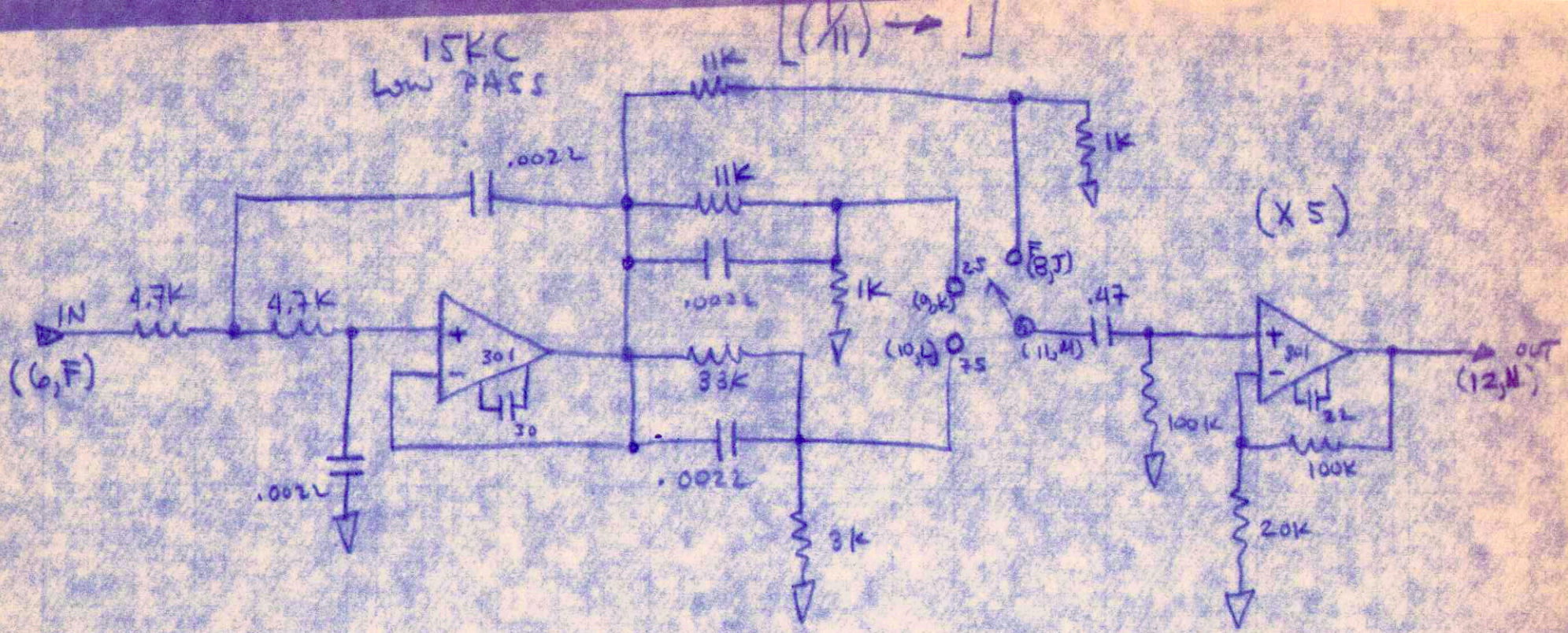

MULTIMETER

SWITCHABLE

EMPHASIS -

PHOTO

3/16/45

